 




成功大學

National Cheng Kung University

Deep learning IC Design




Course Administration

- Instructor: Ing-Chao Lin (林英超)
 - email: iclin@mail.ncku.edu.tw
 - Tel: +8866-2757575 ext. 62553

Course Website:

<http://moodle.ncku.edu.tw>

 
announces and slides will be posted here
submit your homework there






Topics Covered

 - Verilog
- Combinational
- Sequential Circuit Design
- Finite State Design
- Data Path Design
- Synthesizable Verilog
- VLSI Design Flow (EDA Design Flow)
- Arithmetic Circuit
- FPGA + Pynq + Vivado
- Deep Learning Background
- Survey of DNN Development Resource
- DNN Inference Background
- DNN Hardware
- Roofline Model
- DNN Memory Access Model
- Case Study



Textbook & Materials

 
- Verilog
 - Verilog HDL, by Samir Palnitkar
 - Digital Design: With an Introduction to Verilog HDL
- Tutorial on HW Architectures for Deep Neural Networks
 - <http://eyeriss.mit.edu/tutorial.html>
- VLSI
 - Integrated Circuit Design, fourth edition, by N. Weste, and David Harris
- Pynq: <http://www.pynq.io>
- Selected Paper






Prerequisite

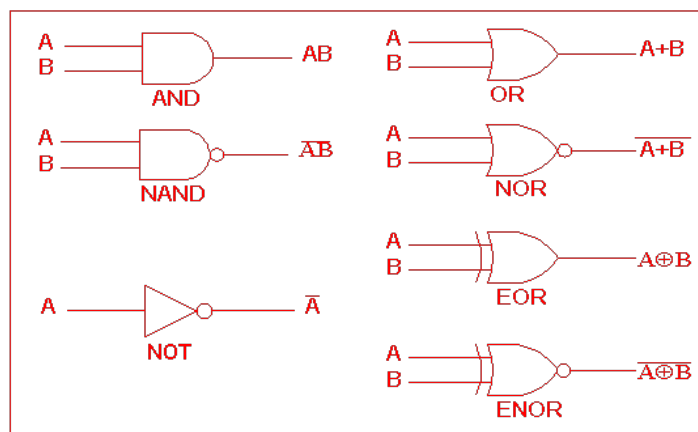- Introduction to Digital System (F720900)
 - Logic Gates and Gate-Level Minimization
 - Combinational Logic and Synchronous Sequential Logic




 - Programming Language: Python
- Personal Computer (Laptop is preferred)



Tentative Grading

 
- Homework and Lab Assignment (35 %)
- Midterm Exams (30 %)
- Class Participation (Attendance and In-class quick test, 15%)
- Paper Presentation (10%)
- Project (10%)
- Percentage of each part may change slightly



Note for Homework and Lab Assignment



 
- Grading for each homework
 - **Report**: You need to carefully explain your codes and results in your results. If your explanation is unclear, you will lose points
- **Honesty is the best policy**. If you copy your homework from someone, **both** will get **zero** points for your homework. In addition, both will lose points of your **final grade** for each violation.






In-class quick test

 
- In-class quick test is a very simple test.
- Will be announced in a few days before. Test what you have learn.
- Normally take less than 20 minutes.
 - If you can't do anything, you will get 40 points
- Cover what I taught in the previous class



 
Recap of basic MOS transistors and logic gates



NMOS

 


PMOS

 


Electric Switch

NMOS TRANSISTOR STRUCTURE

 

 - NMOS = N-channel Metal Oxide Silicon Transistor






nMOS transistor

- When the gate is at a **low** voltage ($V_G=0$):
 - No channel, transistor is off
- When the gate is at a **high** voltage ($V_G=V_{DD}$):
 - Positive voltage inverts a **channel** under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is **ON**

$V_G=0$

 


$G = 0$



OFF


$V_G=V_{DD}$

 

$G = 1$





ON

 

pMOS Transistor


 
 
- Similar, but doping and voltages reversed
 - Input (V_G) at low voltage: transistor **ON**
 - Input (V_G) at high voltage: transistor **OFF**
 - Bubble indicates **inverted** behavior





CMOS Inverter




A	Y
0	
1	0

   



CMOS Inverter




A	Y
0	1
1	0

 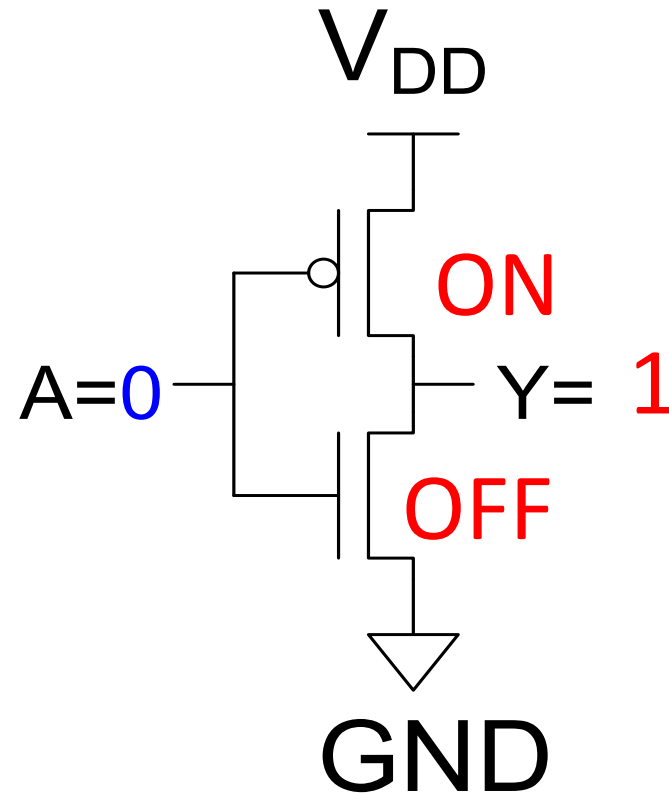 



CMOS NAND Gate-1




A	B	Y
0	0	
0	1	
1	0	
1	1	

   



CMOS NAND Gate-2




A	B	Y
0	0	1
0	1	
1	0	
1	1	

   



CMOS NAND Gate-3




A	B	Y
0	0	1
0	1	1
1	0	
1	1	

   



CMOS NAND Gate-4




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

   



CMOS NAND Gate-5

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 
 
 




Use Switch to build Gates

- CMOS NAND:


A	B	A B	$C = \overline{A B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

   




Use gates to build logic blocks


- Full Adder

 

The Array Multiplier

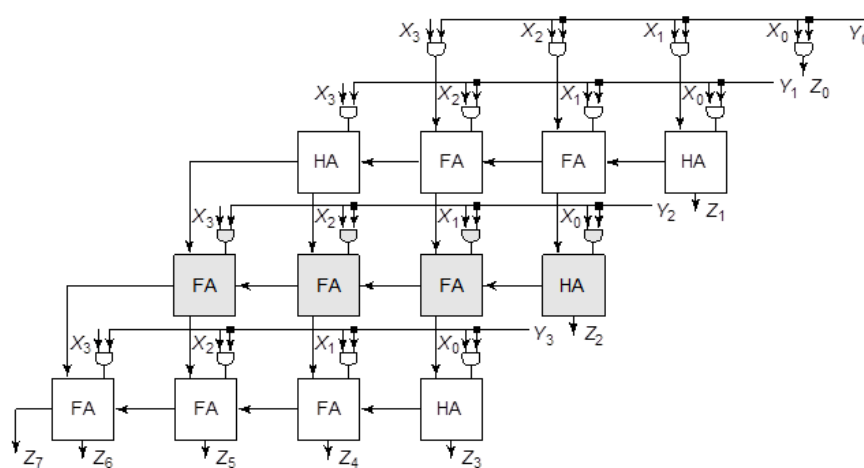


Carry-Save Multiplier

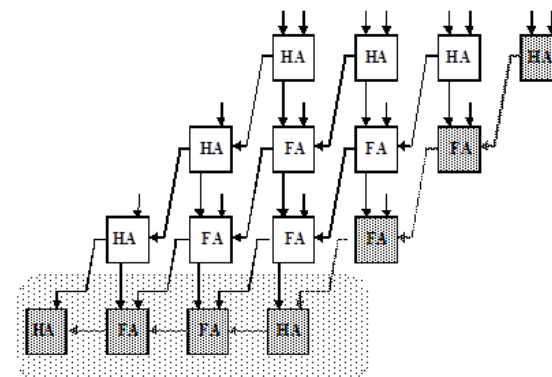


Vector Merging Adder
 
$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$





Use gates to build memory element


 
- Circuit to store 1-bit data
 - SR Latch





- SRAM cell

  

Use logic blocks to build a CPU

 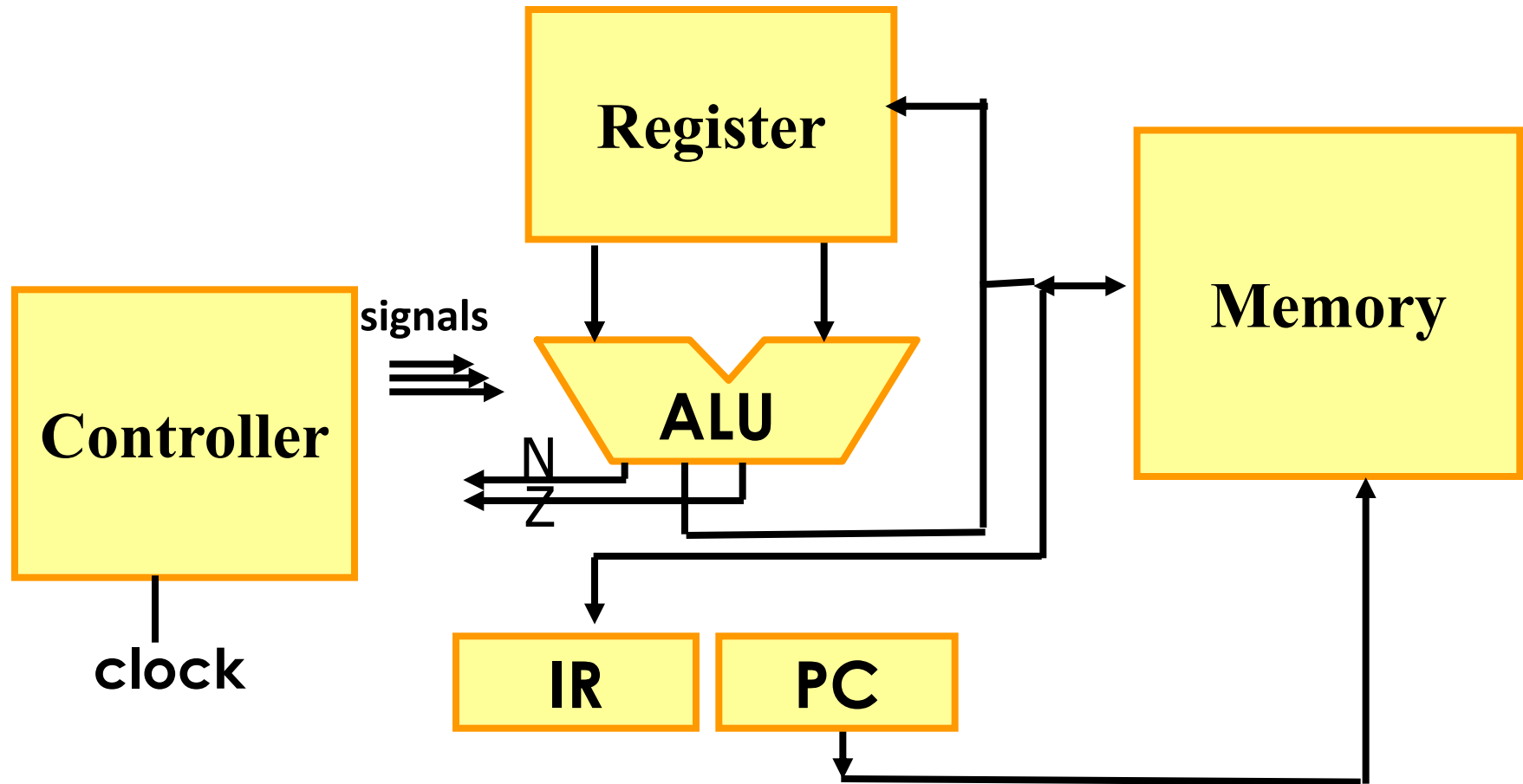

Basic Organization of a Computer

 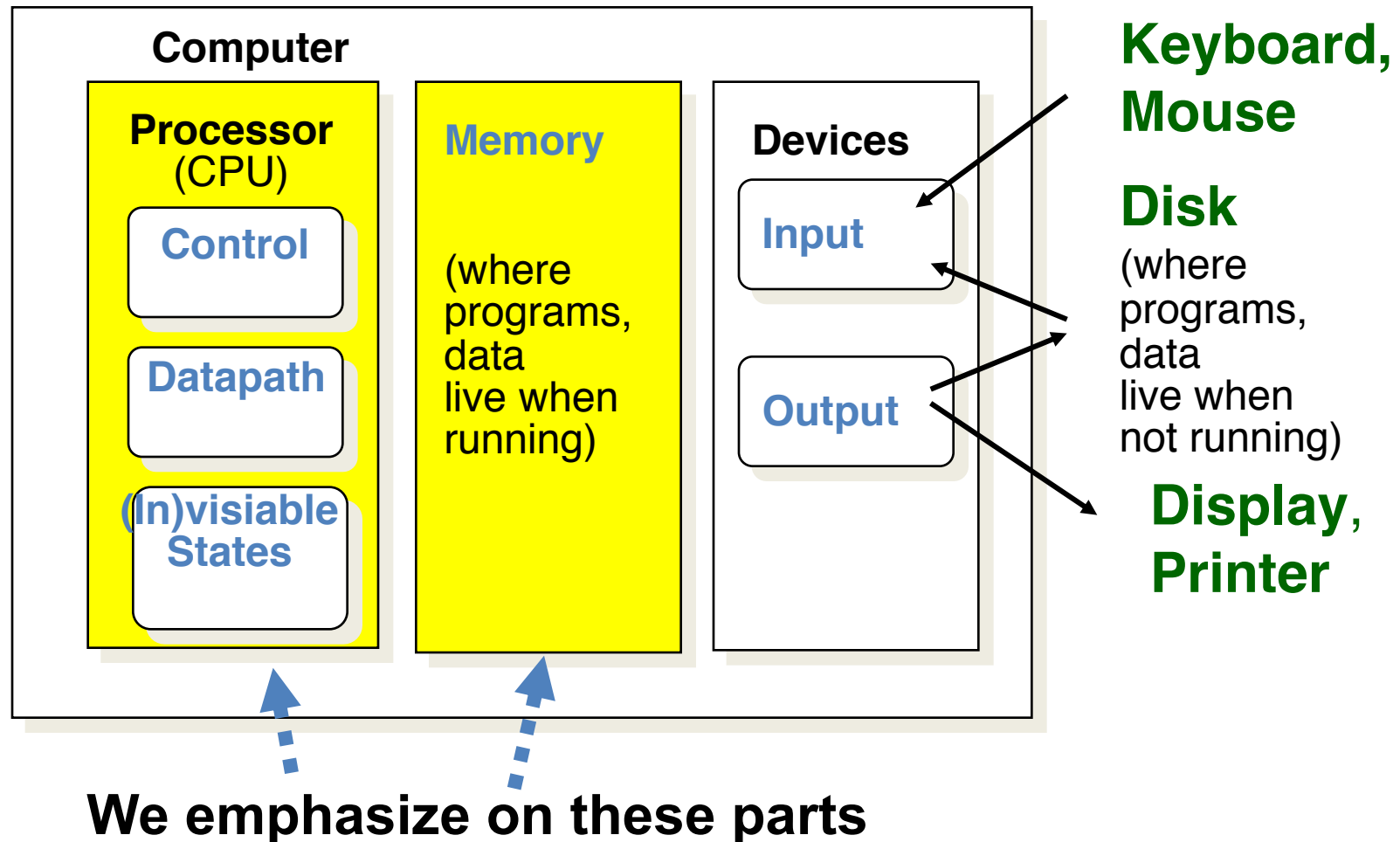



成功大學

National Cheng Kung University

Backup Slides

