



# Combinational Logic Modules

Source:

- Slides partial from Digital System Designs and Practices Using Verilog HDL and FPGAs, Ming-Bo Lin
- Slides partial from Digital IC Design, By Pei-Yin Chen




# Outline

- Combinational Circuits
  - Decoders, and it's implementation
  - Encoders, and it's implementations
  - Priority encoders, and it's implementation
  - Multiplexers, and it's implementation
  - Demultiplexers, and it's implementation
  - Comparators and Magnitude comparators, and it's implementation
  - Describe how to design a parameterized module
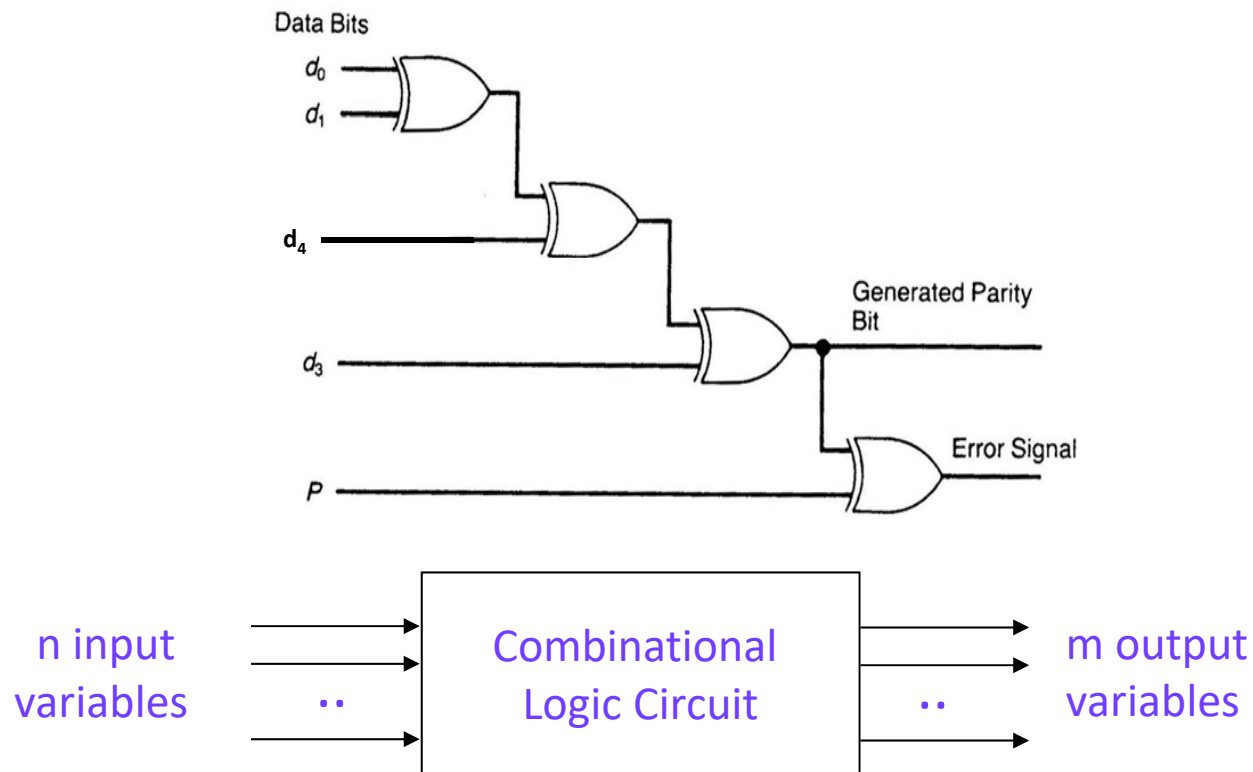
# Combinational Circuit

- A combinational circuit: Outputs at any time are determined directly from the present combination of inputs without regard to previous inputs.



# Example – Alarm (1/2)

Assume that **four** persons might come. Alarm is activated when (1) more than three persons come or (2) the fourth person come together with other persons

```
module four(A , B , C , D , Out);
```

```
input A , B , C , D;
```

```
output Out;
```

```
reg Out , temp;
```

```
always @(A or B or C or D)
```

```
begin
```

```
    case({A , B , C , D})
```

```
        4'b0000: Out = 0;
```

```
        4'b0001: Out = 0;
```

```
        4'b0010: Out = 0;
```

```
        4'b0011: Out = 1;
```

```
        4'b0100: Out = 0;
```

```
        4'b0101: Out = 1;
```

```
        4'b0110: Out = 0;
```

```
        4'b0111: Out = 1;
```

```
        4'b1000: Out = 0;
```

```
        4'b1001: Out = 1;
```

```
        4'b1010: Out = 0;
```

```
        4'b1011: Out = 1;
```

```
        4'b1100: Out = 0;
```

```
        4'b1101: Out = 1;
```

```
        4'b1110: Out = 1;
```

```
        default: Out = 1;
```

```
    endcase
```

```
end
```

```
endmodule
```

*Optimization is done by tools*

A	B	C	D	Out
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

## Example – Alarm (2/2)

```
module four(A , B , C , D);  
input A , B , C , D;  
output Out;  
  
wire t1 , t2 , t3 , t4;  
  
and a1(t1 , A , D);  
and a2(t2 , B , D);  
and a3(t3 , C , D);  
and a4(t4 , A , B , C);  
or o1(Out , t1 , t2 , t3 , t4);  
endmodule
```

CD \ AB	00	01	11	10
00	0	0	1	0
01	0	1	1	0
11	0	1	1	1
10	0	1	1	0

$$\text{Out} = AD + BD + CD + ABC$$


Traditional design method  
(optimization is done by hand)  
→ not suitable for HDL design

# Example - Seven Segment Display

A **BCD** (Binary-Coded Decimal)-to-seven-segment decoder is a combinational circuit that accepts a decimal digit in BCD and generates the appropriate output for selection of segments in a display indicator used for displaying the decimal digit.

The **seven** outputs of the decoder (a, b, c, d, e, f, g) select the corresponding segments in the display as shown in **Fig. (a)**. The numeric designation chosen to represent the decimal digit is shown in **Fig. (b)**.

 Design the BCD-to-seven-segment decoder circuit.



(a) Segment designation




(b) Numerical designation for display

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
...	...	...					...	...		

# Options for Modeling Combinational Logic

- Options for modeling combinational logic:
  - Verilog HDL primitives
    - E.g.: `and` (a, b, c)
  - Continuous assignment
    - E.g.: `assign out = i1 & i2;`
  - Behavioral statement
    - E.g.: `initial`, `always`
  - Interconnected combinational logic modules
  - Combinational UDP (User-defined primitives)
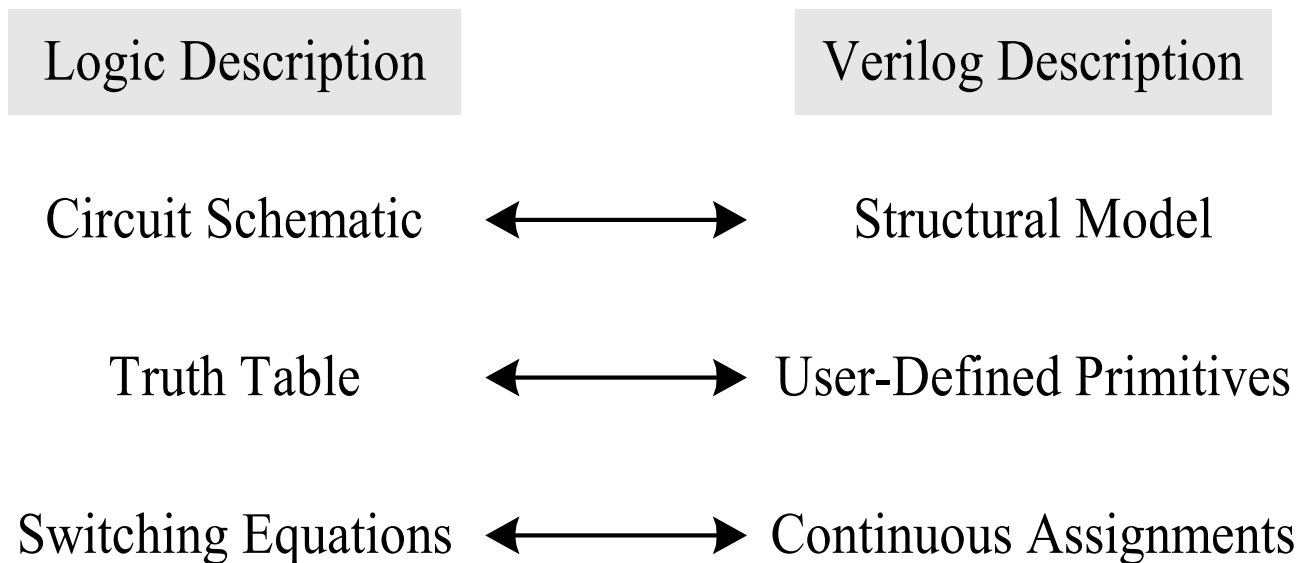
## Three Descriptions of Combination Logic





# UDP example

```
//To be used with the file fulladd.v
```

```
//Primitive name and terminal list
```

```
primitive udp_and(out, a, b);
```

Not Synthesizable

```
//Declarations
```

```
output out; //must not be declared as reg for combinational UDP
```

```
input a, b; //declarations for inputs.
```

```
//State table definition; starts with keyword table
```

```
//The following comment is for readability only
```

```
//Input entries of the state table must be in the
```

```
//same order as the input terminal list.
```

```
table
```

```
  // a  b  :  out;
```

```
    0  0  :  0;
```

```
    0  1  :  0;
```

```
    1  0  :  0;
```

```
    1  1  :  1;
```

```
endtable //end state table definition
```



```
endprimitive //end of udp_and definition
```

# Basic Combinational Logic Modules


- Commonly used combinational logic modules:
  - Decoder
  - Encoder
  - Multiplexer
  - Demultiplexer
  - Comparator
  - Adder (Carry Lookahead Adder)
  - Subtractor
  - Multiplier
  - PLA (Programmable Logic Array)
  - Parity Generator -
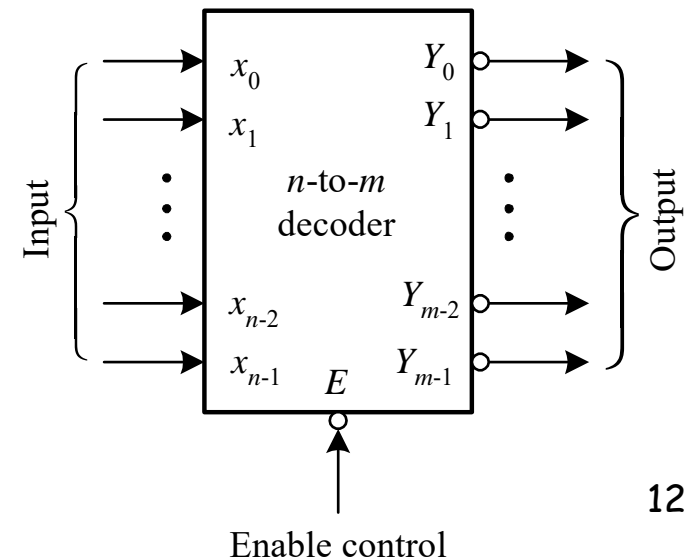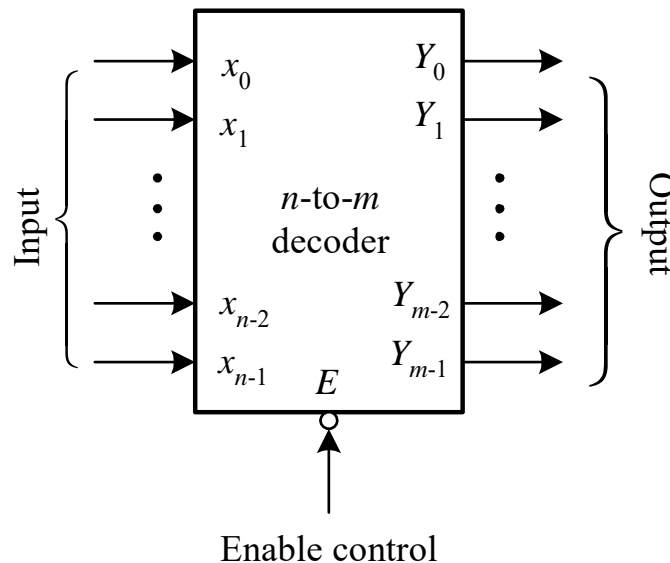
## Decoder Block Diagrams

- An  $n \times m$  decoder has  $n$  input lines and  $m$  output lines. Each output line  $Y_i$  corresponds to the  $i$ th minterm of input (line) variables.
  - **Total** decoding: when  $m = 2^n$ 
    - E.g. (3, 8)
  - **Partial** decoding: when  $m < 2^n$ .




# A 2-to-4 Decoder Example

 

$E$	$x_1$	$x_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
1	$\phi$	$\phi$	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

(b) Function table

 

(c) Logic circuit

# A 2-to-4 Decoder Example

// a 2-to-4 decoder with **active low output**

```
module decoder_2to4_low(x,enable,y);
```

```
input [1:0] x;
```

```
input enable;
```

```
output reg [3:0] y;
```

```
always @(x or enable)
```

```
  if (enable) y = 4'b1111; else
```

```
    case (x)
```

```
      2'b00 : y = 4'b1110;
```

```
      2'b01 : y = 4'b1101;
```


```
      2'b10 : y = 4'b1011;
```

```
      2'b11 : y = 4'b0111;
```

```
      default : y = 4'b1111;
```

```
    endcase
```

```
endmodule
```

 

# A 2-to-4 Decoder with Enable Control

// a 2-to-4 decoder with **active-high output**

```
module decoder_2to4_high(x,enable,y);
```

```
input [1:0] x;
```

```
input enable;
```

```
output reg [3:0] y;
```

```
always @(x or enable)
```

```
if (!enable) y = 4'b0000; else
```

```
case (x)
```

```
2'b00 : y = 4'b0001;
```

```
2'b01 : y = 4'b0010;
```


```
2'b10 : y = 4'b0100;
```

```
2'b11 : y = 4'b1000;
```

```
default : y = 4'b0000;
```

```
endcase
```

```
endmodule
```

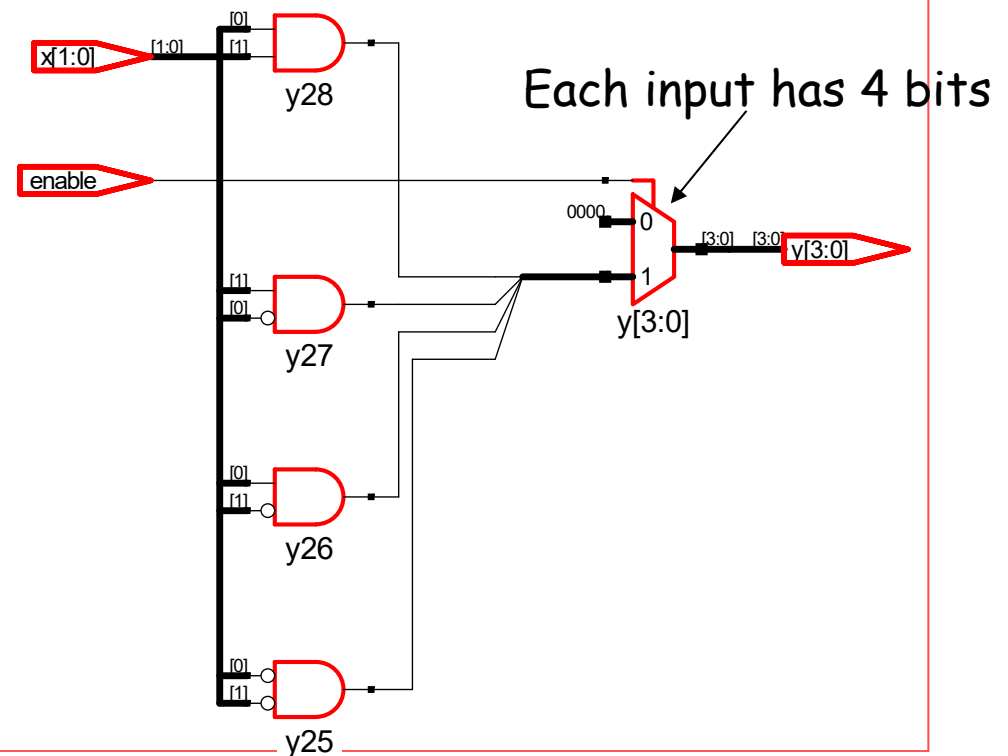


# A Parameterized Decoder Module

```
// an m-to-n decoder with active-high output
module decoder_m2n_high(x,enable,y);
parameter m = 3; // define the number of input lines
parameter n = 8; // define the number of output lines
input [m-1:0] x;
input enable;
output reg [n-1:0] y;
// The body of the m-to-n decoder
always @(x or enable)
    if (!enable) y = {n{1'b0}};
    else        y = {{n-1{1'b0}},1'b1}} << x;
endmodule
```

```
// a 2-to-4 decoder with active-high output
always @(x or enable)
    if (!enable) y = 4'b0000; else
        case (x)
            2'b00 : y = 4'b0001;
            2'b01 : y = 4'b0010;
            2'b10 : y = 4'b0100;
            2'b11 : y = 4'b1000;
            default : y = 4'b0000;
        endcase
endmodule
```

 000=> 00000001 shift 0 bit  
 001=> 00000010 shift 1 bit  
 010=> 00000100 shift 2 bits ....



**Q:** Design an m-to-n decoder with active-low output.



## Expansion of Decoders

- Building a big decoder using small decoders


 



Figure 8.3: A 3-to-8 decoder constructed by cascading two 2-to-4 decoders. -18
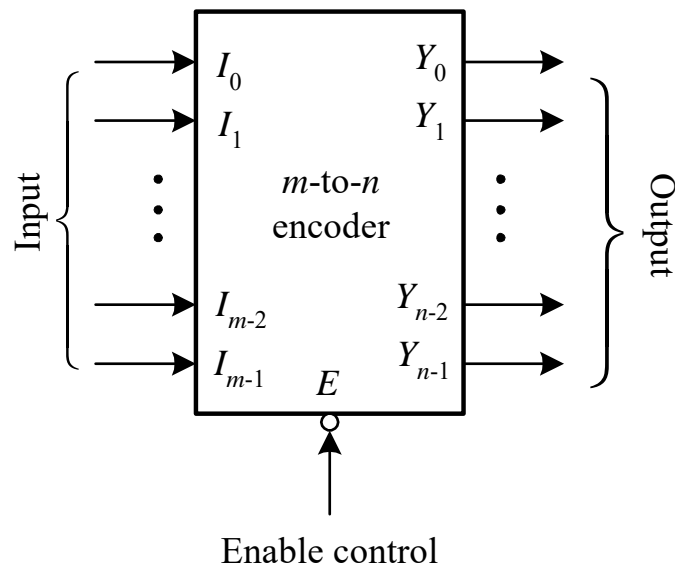
## Encoder Block Diagrams

- An encoder has  $m = 2^n$  (or fewer) **input** lines and  $n$  output lines. The output lines generate the binary code corresponding to the input value.



(a) Noninverted output

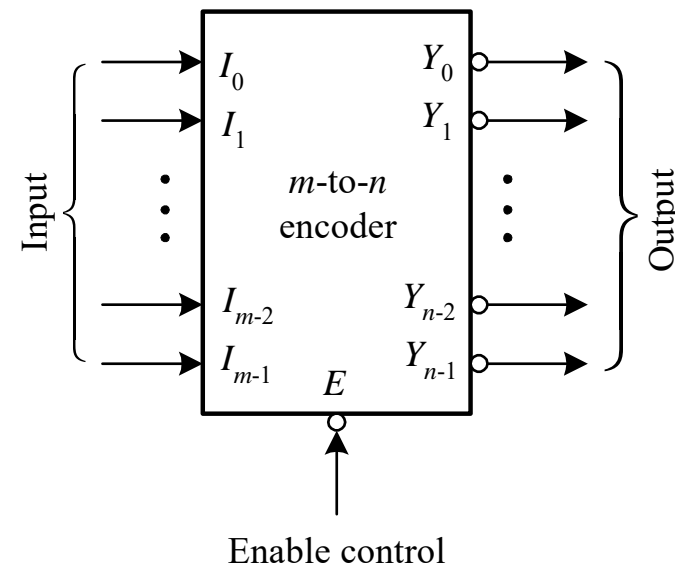


(b) Inverted output

# A 4-to-2 Encoder Example

$I_3$	$I_2$	$I_1$	$I_0$	$Y_1$	$Y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Function table

 


(b) Logic circuit
 
# A 4-to-2 Encoder Example

using **if ... else** structure


```
module encoder_4to2_ifelse(in, y);  
input [3:0] in;  
output reg [1:0] y;  
always @(in) begin  
    if (in == 4'b0001) y = 0; else  
    if (in == 4'b0010) y = 1; else  
    if (in == 4'b0100) y = 2; else  
    if (in == 4'b1000) y = 3; else  
        y = 2'bx;  
end  
endmodule
```


 
# Another 4-to-2 Encoder Example

using **case** structure


```
module encoder_4to2_case(in, y);  
input  [3:0] in;  
output reg [1:0] y;  
always @(in)  
    case (in)  
        4'b0001 : y = 0;  
        4'b0010 : y = 1;  
        4'b0100 : y = 2;  
        4'b1000 : y = 3;  
        default : y = 2'bx;  
    endcase  
endmodule
```


 
# A 4-to-2 Priority Encoder

A priority is associated with the index values of inputs:

Priority  $I_3 \succ I_2 \succ I_1 \succ I_0$




(a) Block diagram

Input				Output	
$I_3$	$I_2$	$I_1$	$I_0$	$A_1$	$A_0$
0	0	0	1	0	0
0	0	1	$\phi$	0	1
0	1	$\phi$	$\phi$	1	0
1	$\phi$	$\phi$	$\phi$	1	1

(b) Function table

# A 4-to-2 Priority Encoder Example

```
// a 4-to-2 priority encoder using if ... else structure
module priority_encoder_4to2_ifelse (in, valid_in, y);
input [3:0] in;
output reg [1:0] y;
output valid_in;
// the body of the 4-to-2 priority encoder
assign valid_in = |in;
always @(in) begin
    if (in[3]) y = 3; else
    if (in[2]) y = 2; else
    if (in[1]) y = 1; else
    if (in[0]) y = 0; else
    y = 2'bx;
end
endmodule
```

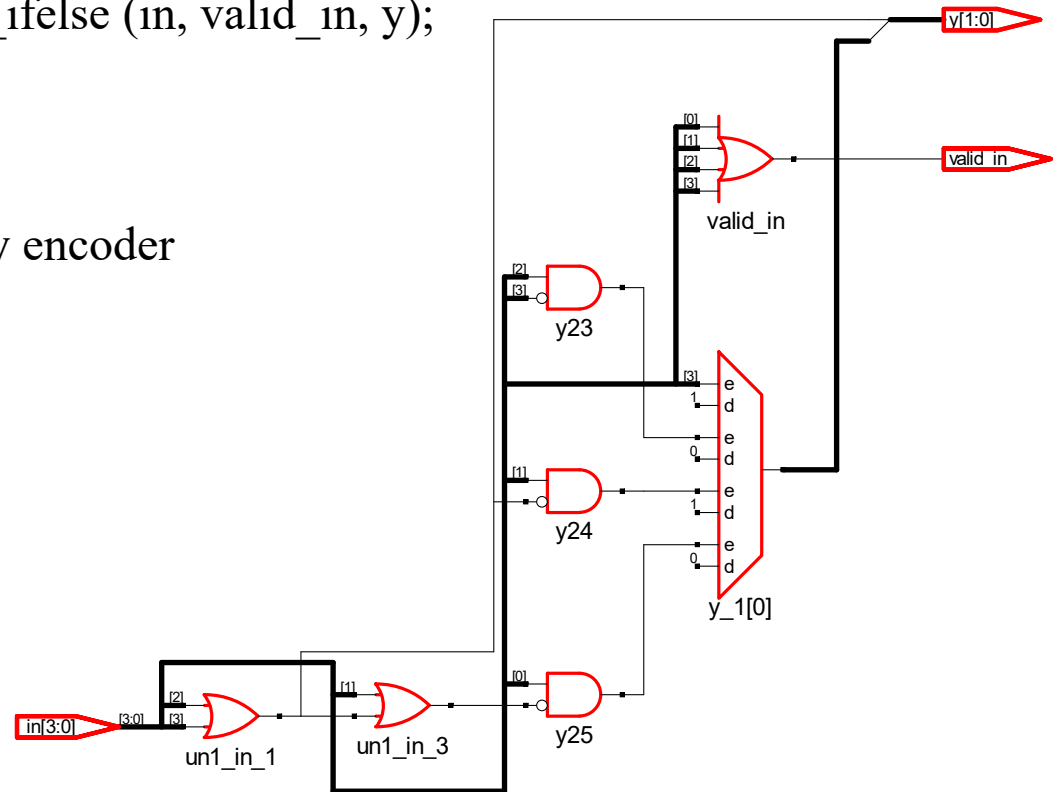


Position 3 has the highest priority

# Another 4-to-2 Priority Encoder Example

```
// a 4-to-2 priority encoder using case structure
module priority_encoder_4to2_case(in, valid_in, y);
input [3:0] in;
output reg [1:0] y;
output valid_in;
// the body of the 4-to-2 priority encoder
assign valid_in = |in;
always @(in) casex (in)
    4'b1xxx: y = 3;
    4'b01xx: y = 2;
    4'b001x: y = 1;
    4'b0001: y = 0;
    default: y = 2'bx;
endcase
endmodule
```

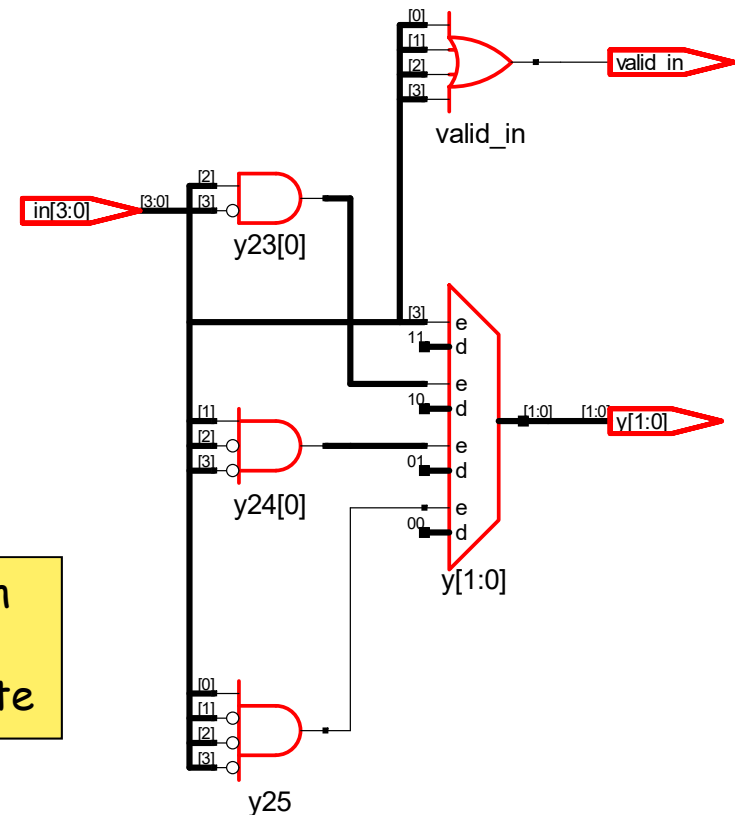Avoid inferring a latch  
because casex  
statement is incomplete



casez : Treats z as don't care.  
casex : Treats x and z as don't care




# An m-to-n Priority Encoder using a for Loop


```
// a parameterized M-to-N priority encoder.
module priencoder_m2n(x, valid_in, y);
parameter M = 8; // define the number of inputs
parameter N = 3; // define the number of outputs
input [M-1:0] x;
output valid_in; // indicates the data input x is valid.
output reg [N-1:0] y;
integer i;
// the body of the M-to-N priority encoder
assign valid_in = |x;
always @(*) begin: check_for_1
    for (i = M - 1 ; i >= 0 ; i = i - 1)
        if (x[i] == 1) begin y = i;
            disable check_for_1; end
        else y = 0;
    end
endmodule
```
 
## Multiplexer Block Diagrams

- An  $m$ -to-1 (  $m = 2^n$  ) multiplexer has  $m$  input lines, 1 output line, and  $n$  selection lines. The input line  $I_i$  selected by the binary combination of  $n$  source selection lines is directed to the output line,  $Y$ .




Without enable control

 

With enable control

# A 4-to-1 Multiplexer Example


Gate-based 4-to-1 multiplexers

 

(a) Logic symbol

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

 


(c) Logic circuit
 
# An $n$ -bit 4-to-1 Multiplexer Example

// an N-bit 4-to-1 multiplexer using **conditional operator**.

```
module mux_nbit_4to1(select, in3, in2, in1, in0, y);  
  parameter N = 4; // define the width of 4-to-1 multiplexer  
  input [1:0] select;  
  input [N-1:0] in3, in2, in1, in0;  
  output [N-1:0] y;  
  // the body of the N-bit 4-to-1 multiplexer  
  assign y = select[1] ?  
    (select[0] ? in3 : in2) :  
    (select[0] ? in1 : in0);  
endmodule
```



Data flow modeling

## The Second $n$ -bit 4-to-1 Multiplexer

// an N-bit 4-to-1 multiplexer with enable control.

```
module mux_nbit_4to1_en (select, enable, in3, in2, in1, in0, y);
parameter N = 4; // define the width of 4-to-1 multiplexer
input [1:0] select;
input enable;
input [N-1:0] in3, in2, in1, in0;
output reg [N-1:0] y;
// the body of the N-bit 4-to-1 multiplexer
always @(select or enable or in0 or in1 or in2 or in3)
    if (!enable) y = {N{1'b0}};
    else y = select[1] ?
        (select[0] ? in3 : in2) :
        (select[0] ? in1 : in0) ;
endmodule
```

Behavioral modeling


# The Third $n$ -bit 4-to-1 Multiplexer

// an N-bit 4-to-1 multiplexer using **case** structure.

```

module mux_nbit_4to1_case(select, in3, in2, in1, in0, y);
parameter N = 8; // define the width of 4-to-1 multiplexer
input [1:0] select;
input [N-1:0] in3, in2, in1, in0;
output reg [N-1:0] y;
// the body of the N-bit 4-to-1 multiplexer
always @(*)
    case (select)
        2'b11: y = in3 ;
        2'b10: y = in2 ;
        2'b01: y = in1 ;
        2'b00: y = in0 ;
    endcase
endmodule

```

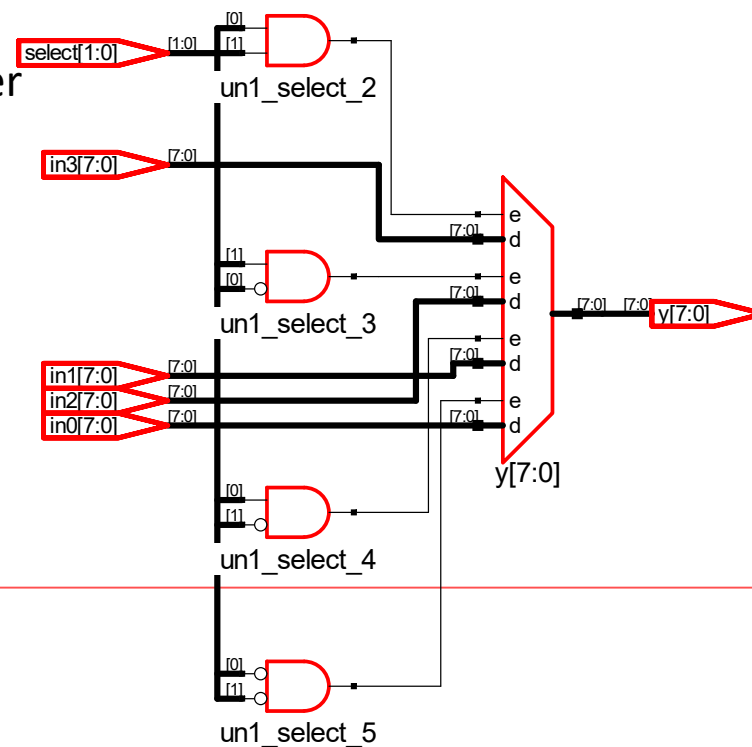


# A Parameterized M-to-1 Multiplexer

```

module mux_m_to_1(select, in, y);
parameter M = 4; // define the size of M-to-1 multiplexer
parameter K = 2; // define the number of selection lines
input [K-1:0] select;
input [M-1:0] in;
output reg y;
// the body of the M-to-1 multiplexer
integer i;
always @(*)
    for (i = 0; i < M; i = i + 1)
        if (select == i) y = in[i];
endmodule

```

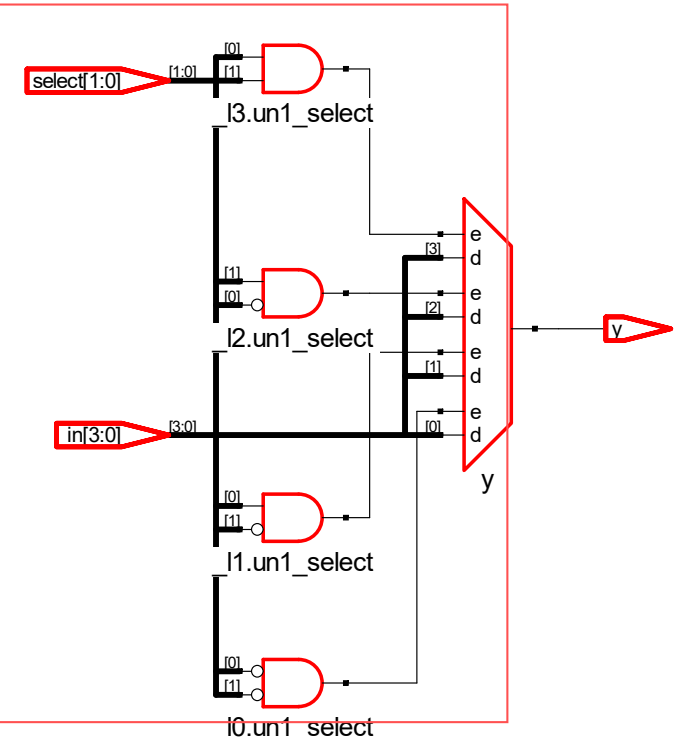


If(select==0) y=in[0]  
 If(select==1) y=in[1]  
 If(select==2) y=in[2]  
 If(select==3) y=in[3]

Q: Explain the philosophy behind this program. Why is it so simple? (*Hint: Please go back to the basic definition of multiplexer.*)
 
# Expansion of Multiplexers

- Two ways to build big mux
  - Straightforward approach** like what we have done
  - Cascading** small multiplexer modules to construct a big mux
- Multiplexer Tree


8-to-1 mux constructed by cascading two 4-to-1 and one 2-to-1 muxes





 
## DeMultiplexer Block Diagrams

- A **1-to- $m$**  (  $m = 2^n$  ) **demultiplexer** has **1** input line,  **$m$**  output lines, and  **$n$**  destination selection lines. The input line  **$D$**  is directed to the output line  **$Y_i$**  selected by the binary combination of  **$n$**  destination selection lines.



Without **enable** control

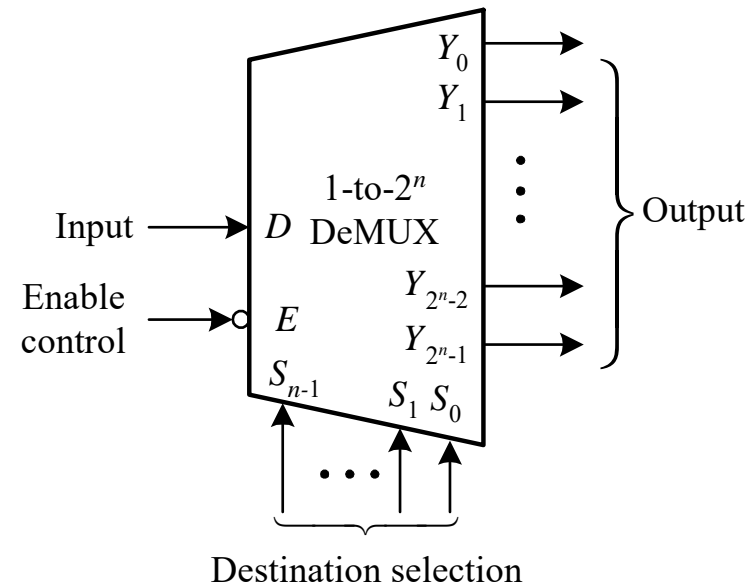


With **enable** control
 
# A 1-to-4 DeMultiplexer Example

Gate-based 1-to-4 demultiplexers


Input **D** is directed to the output **Y**



(a) Logic symbol

$E$	$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
1	$\phi$	$\phi$	0	0	0	0
0	0	0	0	0	0	$D$
0	0	1	0	0	$D$	0
0	1	0	0	$D$	0	0
0	1	1	$D$	0	0	0

(b) Function table

 


(c) Logic circuit
 
# An $n$ -bit 1-to-4 DeMultiplexer Example

An  $N$ -bit 1-to-4 demultiplexer using **if ... else** structure

```
module demux_1to4_ifelse (select, in, y3, y2, y1, y0);  
  parameter N = 4; // define the width of the demultiplexer  
  input  [1:0] select;  
  input  [N-1:0] in;  
  output reg [N-1:0] y3, y2, y1, y0;  
  
  // the body of the N-bit 1-to-4 demultiplexer  
  always @(select or in) begin  
    if (select == 3) y3 = in; else y3 = {N{1'b0}};  
    if (select == 2) y2 = in; else y2 = {N{1'b0}};  
    if (select == 1) y1 = in; else y1 = {N{1'b0}};  
    if (select == 0) y0 = in; else y0 = {N{1'b0}};  
  end  
endmodule
```



# The Second $n$ -bit 1-to-4 DeMultiplexer with **Enable** control

An N-bit 1-to-4 demultiplexer using **if ... else** structure with Enable control

```
module demux_1to4_ifelse_en(select, enable, in, y3, y2, y1, y0);
parameter N = 4;    // Define the width of the demultiplexer
input  [1:0] select;
input  enable;
input  [N-1:0] in;
output reg [N-1:0] y3, y2, y1, y0;
// the body of the N-bit 1-to-4 demultiplexer
always @(select or in or enable) begin
    if (enable)begin
        if (select == 3) y3 = in; else y3 = {N{1'b0}};
        if (select == 2) y2 = in; else y2 = {N{1'b0}};
        if (select == 1) y1 = in; else y1 = {N{1'b0}};
        if (select == 0) y0 = in; else y0 = {N{1'b0}};
    end else begin
        y3 = {N{1'b0}}; y2 = {N{1'b0}}; y1 = {N{1'b0}}; y0 = {N{1'b0}}; end
    end
endmodule
```


# n-bit 1-to-4 DeMultiplexer using **case** struct

```
module demux_1to4_case (select, in, y3, y2, y1, y0);
parameter N = 4; // define the width of the demultiplexer
input  [1:0] select;
input  [N-1:0] in;
output reg [N-1:0] y3, y2, y1, y0;

// the body of the N-bit 1-to-4 demultiplexer
always @(select or in) begin
    y3 = {N{1'b0}}; y2 = {N{1'b0}};
    y1 = {N{1'b0}}; y0 = {N{1'b0}};
    case (select)
        2'b11: y3 = in;
        2'b10: y2 = in;
        2'b01: y1 = in;
        2'b00: y0 = in;
    endcase
end
endmodule
```

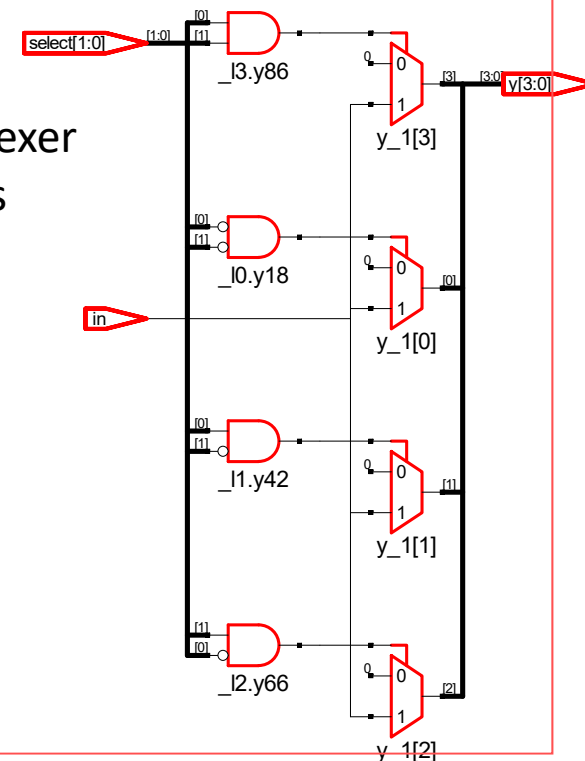
# A Parameterized DeMultiplexer Example

```
// an example of 1-to-M demultiplexer module
module demux_1_to_m(select, in, y);
parameter M = 4; // define the size of 1-to-m demultiplexer
parameter K= 2; // define the number of selection lines
input [K-1:0] select;
input in;
output reg [M-1:0] y;
integer i;
// the body of the 1-to-M demultiplexer
always @(*)
    for (i = 0; i < M; i = i + 1) begin
        if (select == i) y[i] = in; else y[i] = 1'b0; end
    endmodule
```



 
## DeMux vs. Decoder

- A 1-to-4 demux may function as a 2-to-4



S1	S0	Y3	y2	Y1	y0
0	0	0	0	0	D
0	1	0	0	D	0
1	0	0	D	0	0
1	1	D	0	0	0

 

x1	x0	Y3	y2	Y1	y0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Set D to 1, become a decoder


## Question

- Convert a 1-to-8 demux may function as a 3-to-8 decoder



 
# DeMux (with enable) vs. Decoder

- In 1-to-4 Demux become a 2-to-4 decoder
- ➔ If data input is set to 1 and has enable control



Set **D** to 1

 


$E$	$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
1	$\phi$	$\phi$	0	0	0	0
0	0	0	0	0	0	$D$
0	0	1	0	0	$D$	0
0	1	0	0	$D$	0	0
0	1	1	$D$	0	0	0

**D=1**

$E$	$S_1$	$S_0$	$Y_3$	$y_2$	$Y_1$	$y_0$
1	X	X	0	0	0	0
0	0	0	0	0	0	1
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	1	0	0	0

 
## Expansion of DeMux

- A **big** DeMux, such as 1-to-128, may be needed
- A 1-to-8 DeMux constructed by cascading two 1-to-4 and one 1-to-2 DeMux
- Using **case** or **if-else statement** or demultiplexer tree


 
# Comparators


- **Equality** comparators:
  - Determine whether two numbers are equal
  - using **n-bit XOR gate**
- **Magnitude** comparator:
  - Determines the relative magnitude of two numbers
- Two types of magnitude comparator circuits:
  - **Comparator**
  - Cascadable comparator



A 4-bit cascadable comparator block diagram
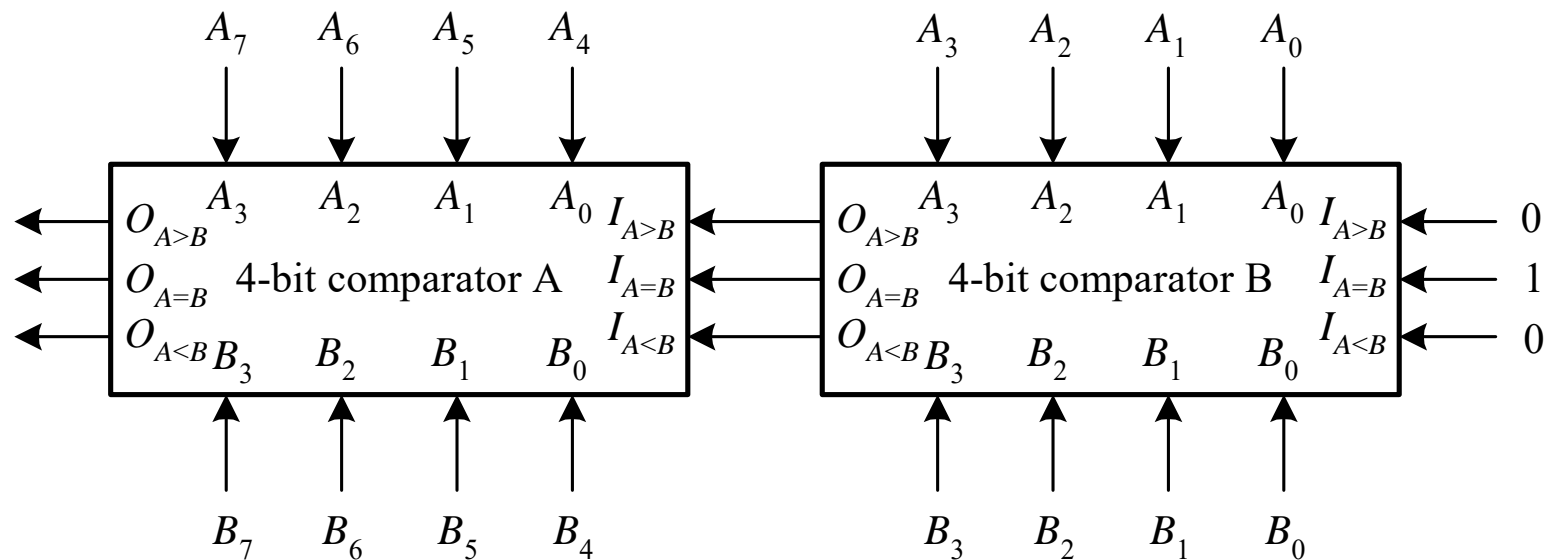
# Comparators

- Cascading two 4-bit comparators to form an 8-bit comparator.




• What will happen if you set the input value (010) at the rightmost end to other values?
 
# A Comparator Example

an N-bit comparator module example

```
module comparator_simple(a, b, cgt, clt, ceq);  
parameter N = 4; // define the size of comparator  
  
// I/O port declarations  
input [N-1:0] a, b;  
output cgt, clt, ceq;  
  
// the body of the N-bit comparator  
assign cgt = (a > b);  
assign clt = (a < b);  
assign ceq = (a == b);  
endmodule
```




# A Cascadable Comparator Example

```

module comparator_cascadable (Iagtb, Iaeqb, Ialtb, a, b, Oagtb, Oaeqb, Oaltb);
parameter N = 4; // define the size of comparator
// I/O port declarations
input  Iagtb, Iaeqb, Ialtb, input  [N-1:0] a, b;
output Oagtb, Oaeqb, Oaltb;

// dataflow modeling using relation operators
assign Oaeqb = (a == b) && (Iaeqb == 1); // equality
assign Oagtb = (a > b) || ((a == b) && (Iagtb == 1)); // greater than
assign Oaltb = (a < b) || ((a == b) && (Ialtb == 1)); // less than
endmodule



```

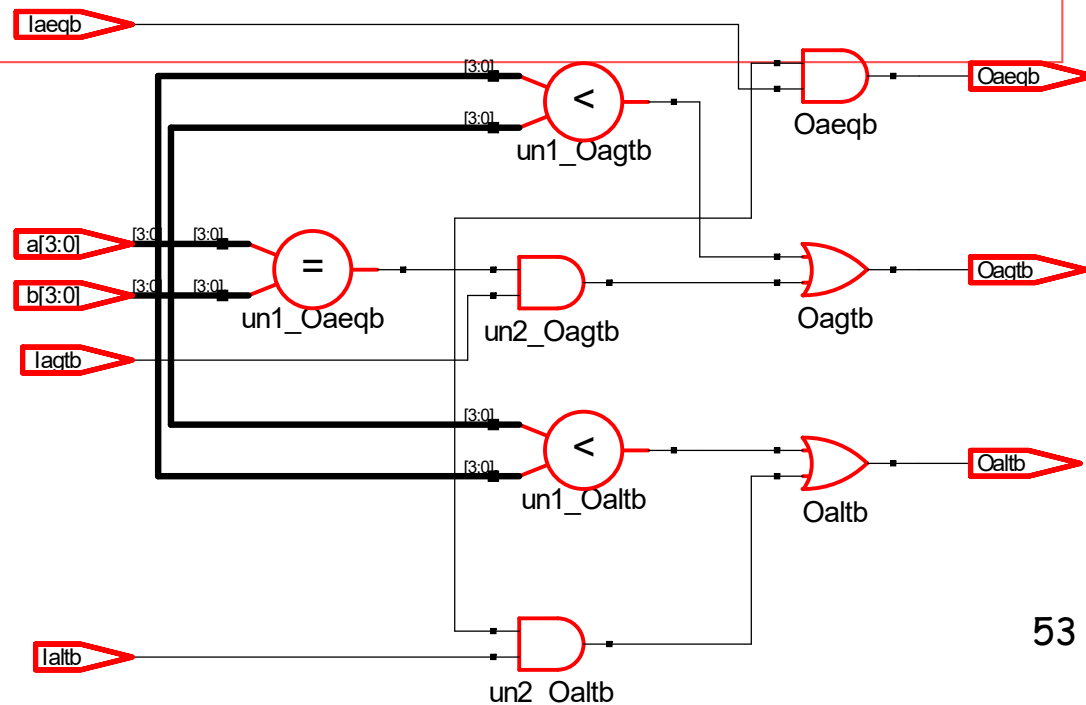
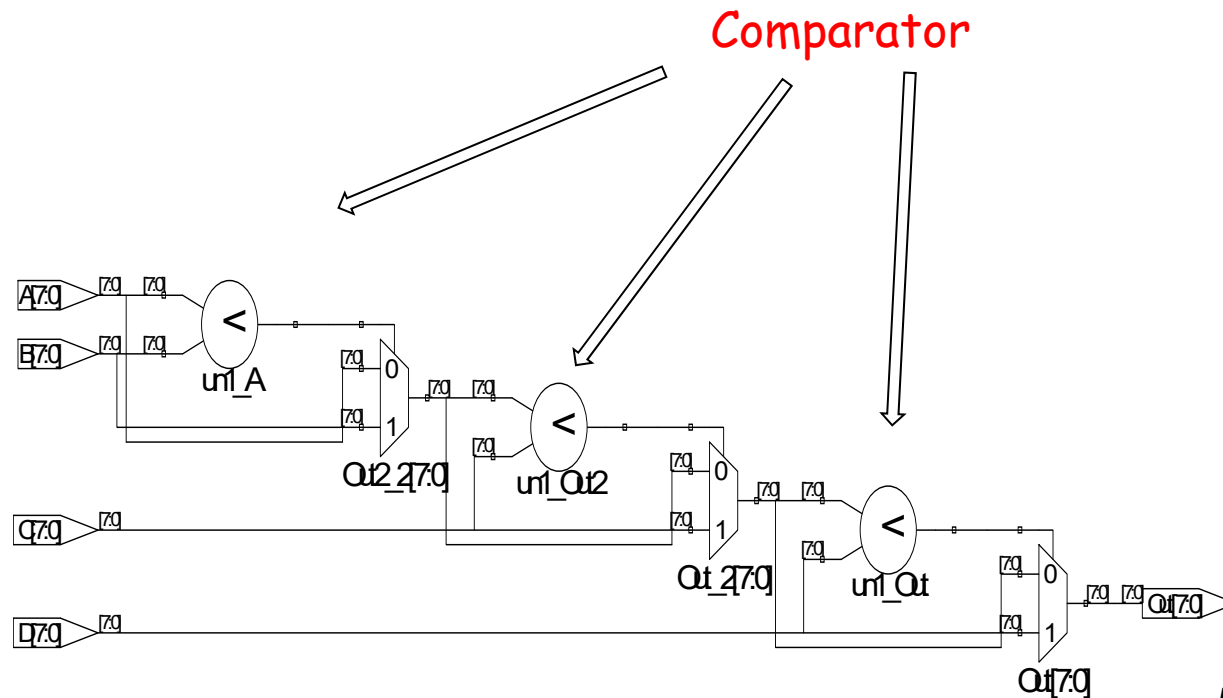 
# Delay of Comparator

Decide the **biggest** value among A, B, C, and D.

```
Method_1 ( (3 stages):
always @(A or B or C or D)
begin
    if(A >= B)
        Out1=A;
    else
        Out1=B;
    if(Out1 >= C)
        Out2=Out1;
    else
        Out2=C;
    if(Out2 >= D)
        Out=Out2;
    else
        Out=D;
end
```



# Delay of Comparator

Decide the biggest value among A, B, C, and D.

Method\_2: (hierarchical tree structure, 2 stage)

always @(A or B or C or D)

begin

if(A >= B)

Out1=A;

else

Out1=B;

if(C >= D)

Out2=C;

else

Out2=D;



if(Out1 >= Out2)

Out=Out1;

else



Out=Out2;

end

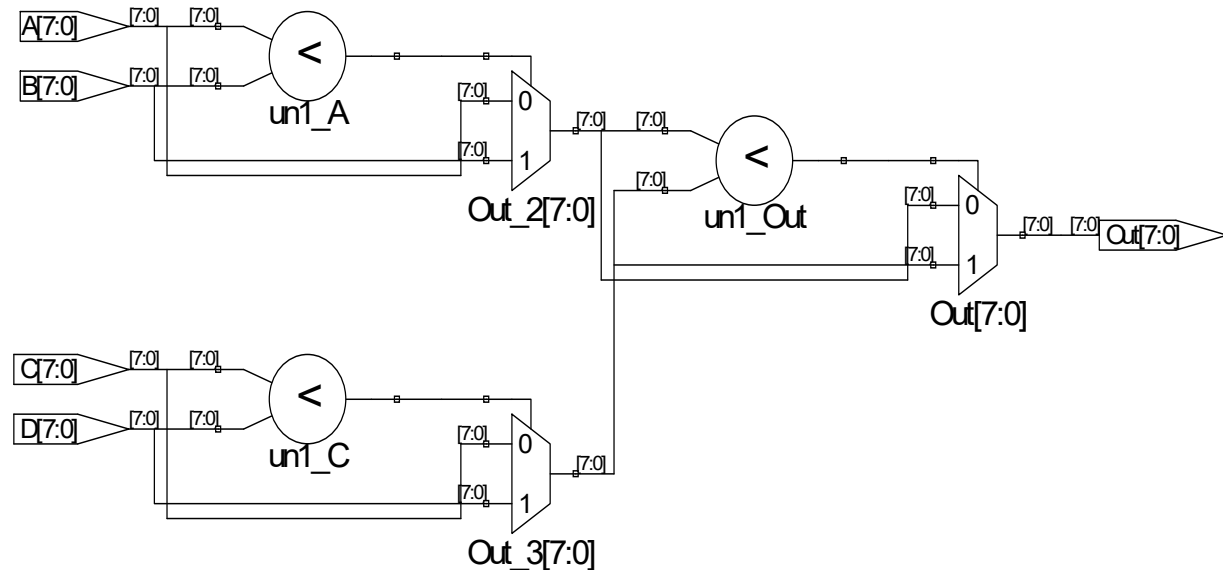 



# Delay of Comparator

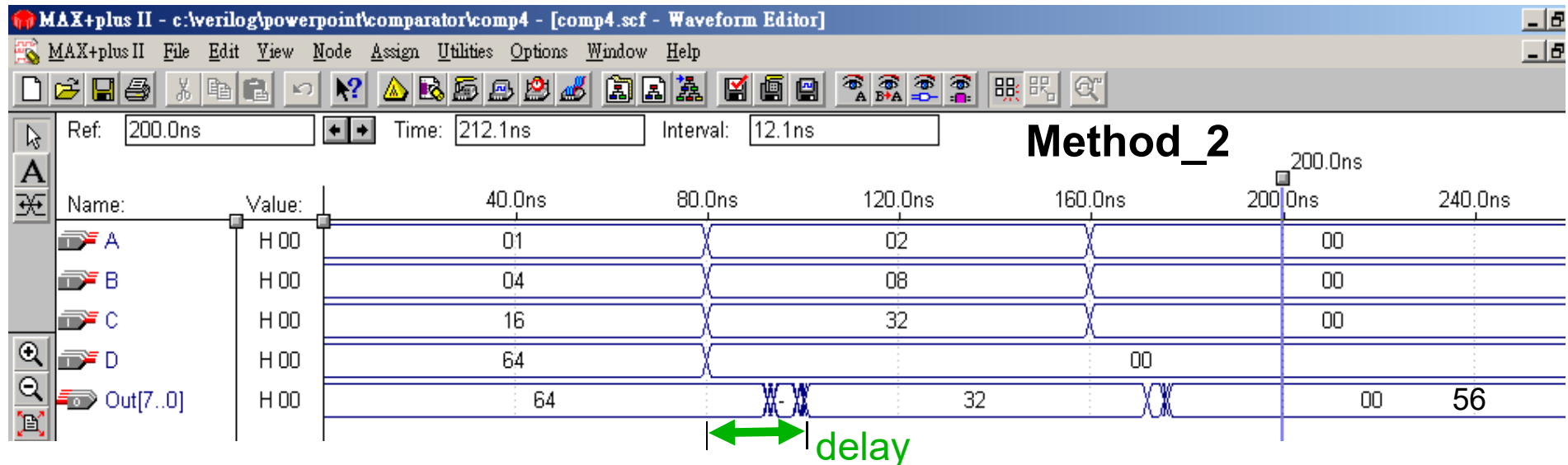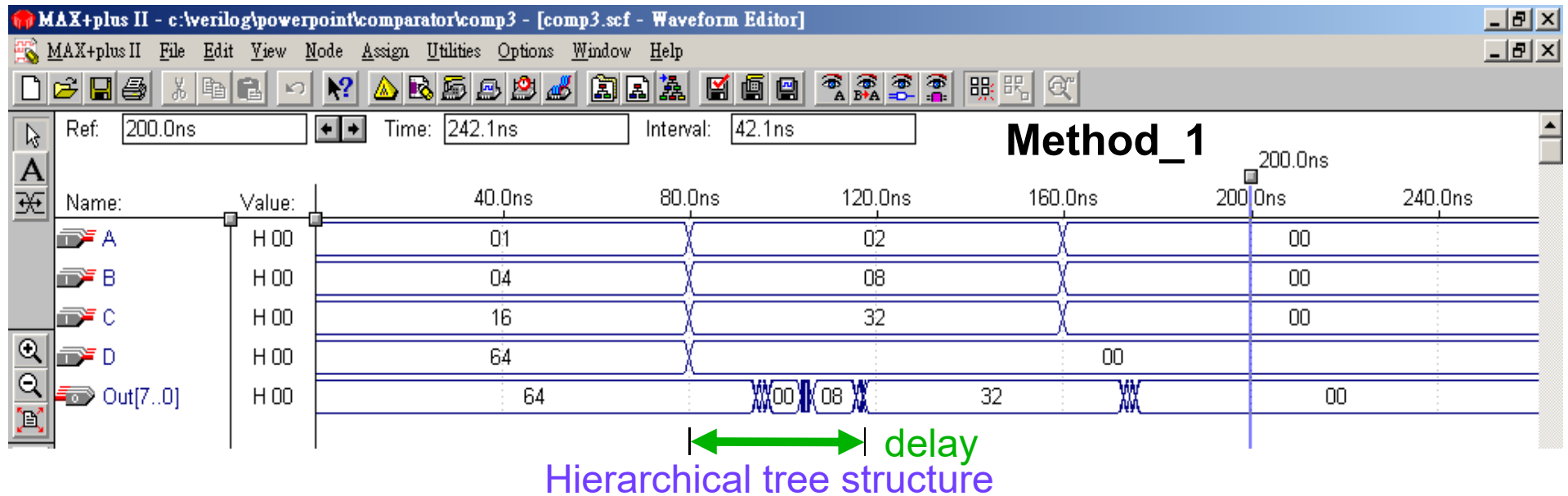

# Arithmetic Logic Unit (1/2)

S4 S3 S2 S1 S0 Cin	Operation	Function	Implementation
0 0 0 0 0 0	$Y \leq A$	Transfer A	Arithmetic Unit
0 0 0 0 0 1	$Y \leq A + 1$	Increment A	Arithmetic Unit
0 0 0 0 1 0	$Y \leq A + B$	Addition	Arithmetic Unit
0 0 0 0 1 1	$Y \leq A + B + 1$	Add with carry	Arithmetic Unit
0 0 0 1 0 0	$Y \leq A + \overline{B}$	A plus 1's complement of B	Arithmetic Unit
0 0 0 1 0 1	$Y \leq A + \overline{B} + 1$	Subtraction	Arithmetic Unit
0 0 0 1 1 0	$Y \leq A - 1$	Decrement A	Arithmetic Unit
0 0 0 1 1 1	$Y \leq A$	Transfer A	Arithmetic Unit
0 0 1 0 0 0	$Y \leq A \text{ and } B$	AND	Logic Unit
0 0 1 0 1 0	$Y \leq A \text{ or } B$	OR	Logic Unit
0 0 1 1 0 0	$Y \leq A \text{ xor } B$	XOR	Logic Unit
0 0 1 1 1 0	$Y \leq \overline{A}$	Complement A	Logic Unit
0 0 0 0 0 0	$Y \leq A$	Transfer A	Shifter Unit
0 1 0 0 0 0	$Y \leq \text{shl } A$	Shift left A	Shifter Unit
1 0 0 0 0 0	$Y \leq \text{shr } A$	Shift right A	Shifter Unit
1 1 0 0 0 0	$Y \leq 0$	Transfer 0's	Shifter Unit

# Arithmetic Logic Unit (2/2)

```
module alu_case2(Sel,CarryIn,A,B,Y);  
  input [4:0] Sel;  
  input CarryIn;  
  input [7:0] A,B;  
  output [7:0] Y;  
  reg [7:0] Y;  
  
  always@(Sel or A or B or CarryIn)  
  begin  
    case({Sel[4:0],CarryIn})  
      6'b000000 : Y = A;  
      6'b000001 : Y = A + 1;  
      6'b000010 : Y = A + B;  
      6'b000011 : Y = A + B + 1;  
      6'b000100 : Y = A + !B;  
      6'b000101 : Y = A + !B + 1;  
      6'b000110 : Y = A - 1;  
      6'b000111 : Y = A;  
      6'b001000 : Y = A & B;  
      6'b001010 : Y = A | B;  
      6'b001100 : Y = A ^ B;  
      6'b001110 : Y = !A;  
      6'b010000 : Y = A << 1;  
      6'b100000 : Y = A >> 1;  
      6'b110000 : Y = 0;  
      default: Y = 8'bX;  
    endcase  
  end  
endmodule
```


# Example for IF (1/4)

- Good style takes advantage of “if-else” priority to **synthesize** correct logic

Bad

```
case (STATE)
  IDLE:
    if (LATE == 1'b1)
      ADDR_BUS <= ADDR_MAIN;
    else
      ADDR_BUS <= ADDR_CNTL;
  INTERRUPT:
    if (LATE == 1'b1)
      ADDR_BUS <= ADDR_MAIN;
    else
      ADDR_BUS <= ADDR_INT;
  ....


```

 

Good

```
if (LATE == 1'b1)
  ADDR_BUS <= ADDR_MAIN;
else
  case (STATE)
    IDLE:
      ADDR_BUS <= ADDR_CNTL;
    INTERRUPT:
      ADDR_BUS <= ADDR_INT;
    ....

```

 

## Example for IF (2/4)

```
module style_bad(In_Data, State,  
Out_Data, En);  
input En;  
input [1:0] State;  
input [2:0] In_Data;  
output [3:0] Out_Data;  
reg [3:0] Out_Data;  
parameter A1=0, A2=1, A3=2, A4=3;
```

Bad Style

```
always @(In_Data or State or En)  
begin  
    case(State)  
        A1:  
            begin  
                if(En)  
                    Out_Data = In_Data;  
                else  
                    Out_Data = In_Data - 1;  
            end  
    end
```

```
        A2:  
            begin  
                if(En)  
                    Out_Data = In_Data;  
                else  
                    Out_Data = In_Data + 1;  
            end  
        A3:  
            begin  
                if(En)  
                    Out_Data = In_Data;  
                else  
                    Out_Data = In_Data - 2;  
            end  
        A4:  
            begin  
                if(En)  
                    Out_Data = In_Data;  
                else  
                    Out_Data = In_Data + 2;  
            end  
    endcase end endmodule
```

# Example for IF (3/4)

## Good Style

```
module style_good(In_Data, State, Out_Data, En);  
input En;  
input [1:0] State;  
input [2:0] In_Data;  
output [3:0] Out_Data;  
reg [3:0] Out_Data;
```

```
parameter A1=0, A2=1, A3=2, A4=3;
```


```
always @(In_Data or State or En)  
begin
```

```
    if(En)  
        Out_Data = In_Data;  
    else  
        begin
```


```
        case(State)  
            A1: Out_Data = In_Data - 1;  
            A2: Out_Data = In_Data + 1;  
            A3: Out_Data = In_Data - 2;  
            A4: Out_Data = In_Data + 2;  
        endcase  
    end  
end  
endmodule
```

# Example for IF (4/4)

Bad Style

 

Good Style

 

# Summary

- We studied the following circuits
  - Decoder
  - Encoder
  - Multiplexer
  - Demultiplexer
  - Comparator
  - ALU





Backup Slides