



# CMOS VLSI Design

## MOS Transistor and Logic

# Introduction


---

- **Integrated circuits**: many transistors on one chip.
- *Very Large Scale Integration (VLSI)*: very many >10K gates in a chip
- *Complementary Metal Oxide Semiconductor (CMOS)*
  - Fast, cheap, low power transistors
- Today: How to build your own simple CMOS chip
  - CMOS transistors
  - Building logic gates from transistors
  - Transistor layout and fabrication
- Rest of the course: How to build a good CMOS chip
 
# Silicon Lattice

---



- Transistors are built on a silicon substrate
- Silicon is a **Group IV** material
- Forms crystal lattice with bonds to **four** neighbors


  
# Dopants


---

- Silicon is a semiconductor
- Pure silicon has no free carriers and conducts poorly
- Adding **dopants** increases the conductivity
- Group **V**: extra **electron** (**n-type**)
- Group **III**: missing electron, called **hole** (**p-type**)




 
# p-n Junctions

- A junction between **p-type** and **n-type** semiconductor forms a diode.
- Current flows only in **one** direction




anode

cathode

  


anode

cathode

 

 
# nMOS Transistor

- Four terminals: **gate**, **source**, **drain**, **body**
- Source and drain: n type
  - n+ mean it is heavily doped
- Body: p type
- Gate is used to control the transistor




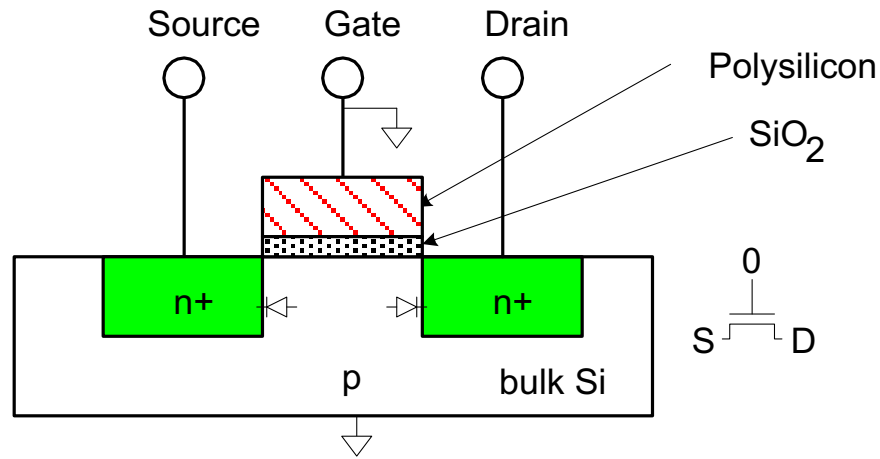
# nMOS Operation ( $V_G=0V$ )

- Body is commonly tied to ground (0 V)
- When the **gate** is at a **low** voltage ( $V_G=0V$ ):
  - P-type body is at low voltage
  - Source-body and drain-body diodes are **OFF**
  - No current flows, transistor is **OFF**


 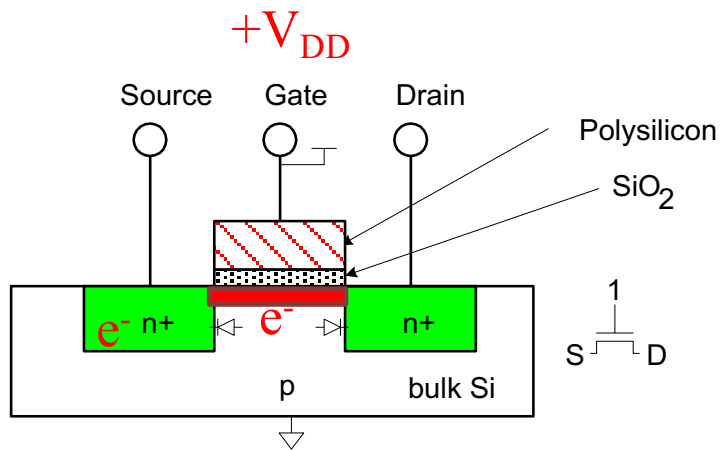
# nMOS Operation ( $V_G=V_{DD}$ )



- When the gate is at a **high** voltage ( $V_G=V_{DD}$ ):
  - **Positive** charge on gate of MOS capacitor
  - Negative charge attracted to body
  - Inverts a channel under gate to n-type
  - Now current can flow through n-type silicon from source through channel to drain, transistor is **ON**




  
# pMOS Transistor

- Similar, but doping and voltages reversed
  - Body tied to high voltage ( $V_{DD}$ )
  - Gate low: transistor **ON**
  - Gate high: transistor **OFF**
  - Bubble indicates **inverted** behavior



# Power Supply Voltage


---

- $GND = 0\text{ V}$
- In 1980's,  $V_{DD} = 5\text{V}$
- $V_{DD}$  has decreased in modern processes
  - High  $V_{DD}$  would damage modern tiny transistors
  - Lower  $V_{DD}$  saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$
 
# Summary: Transistors as Switches

---



- We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain



# CMOS Inverter



---

A	Y
0	
1	

  



# CMOS Inverter

A	Y
0	
1	0

  



# CMOS Inverter

A	Y
0	1
1	0

  



# CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  

# CMOS NAND Gate



A	B	Y
0	0	1
0	1	
1	0	
1	1	

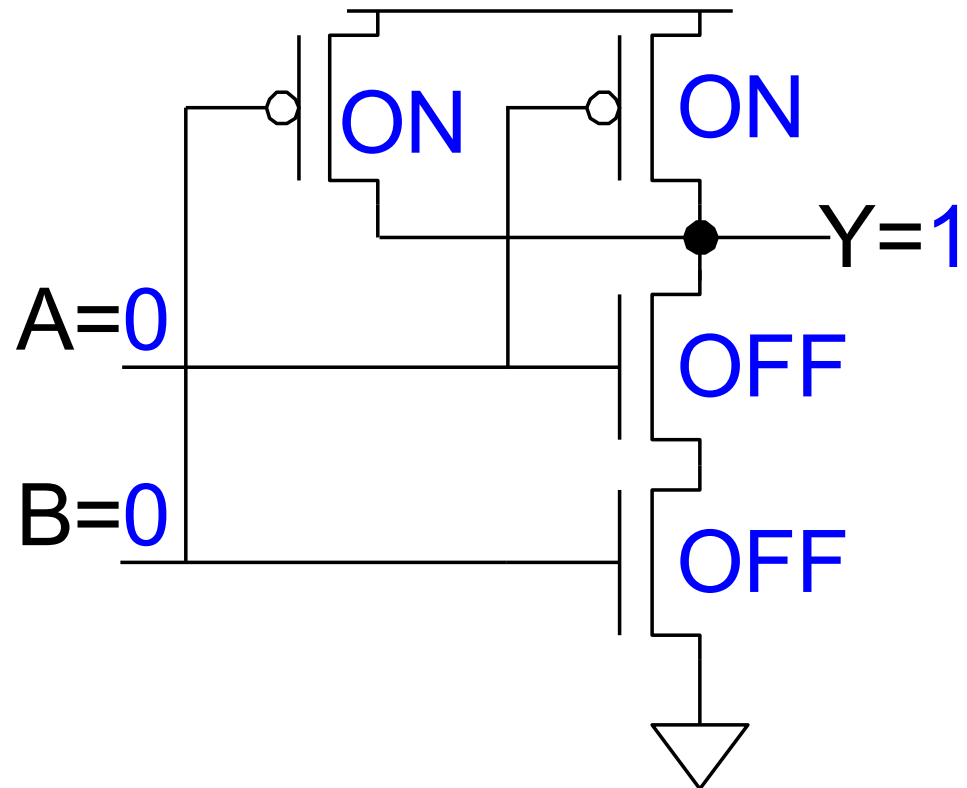 





# CMOS NAND Gate

A	B	Y
0	0	1
<b>0</b>	<b>1</b>	<b>1</b>
1	0	
1	1	

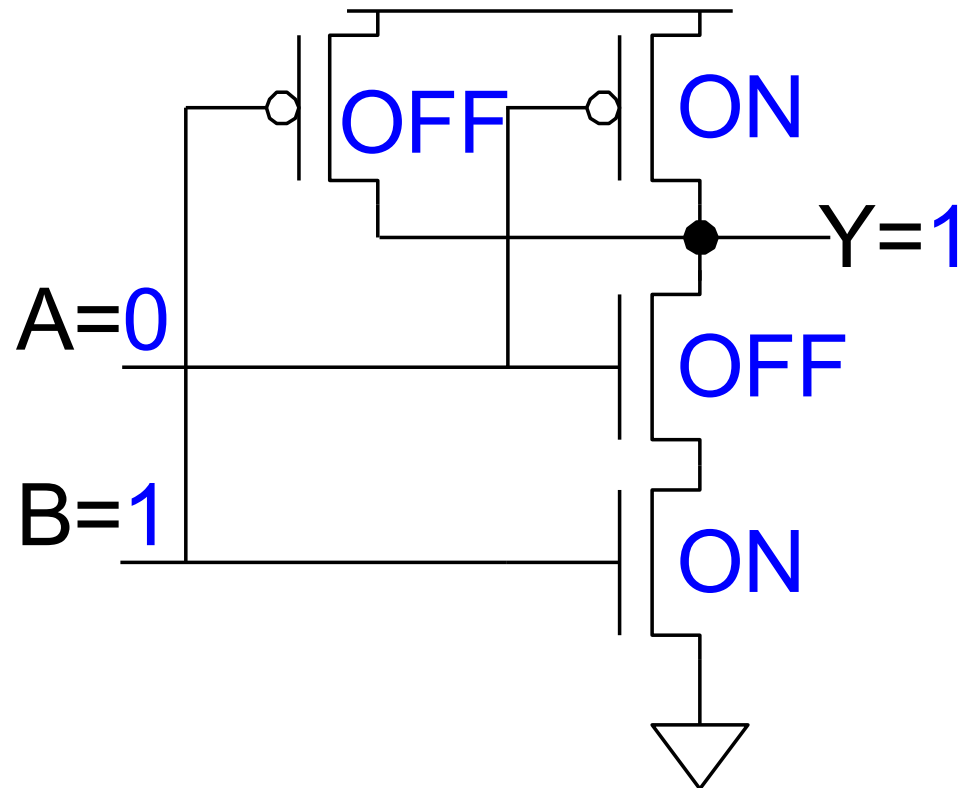 



# CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

  



# CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
<b>1</b>	<b>1</b>	<b>0</b>

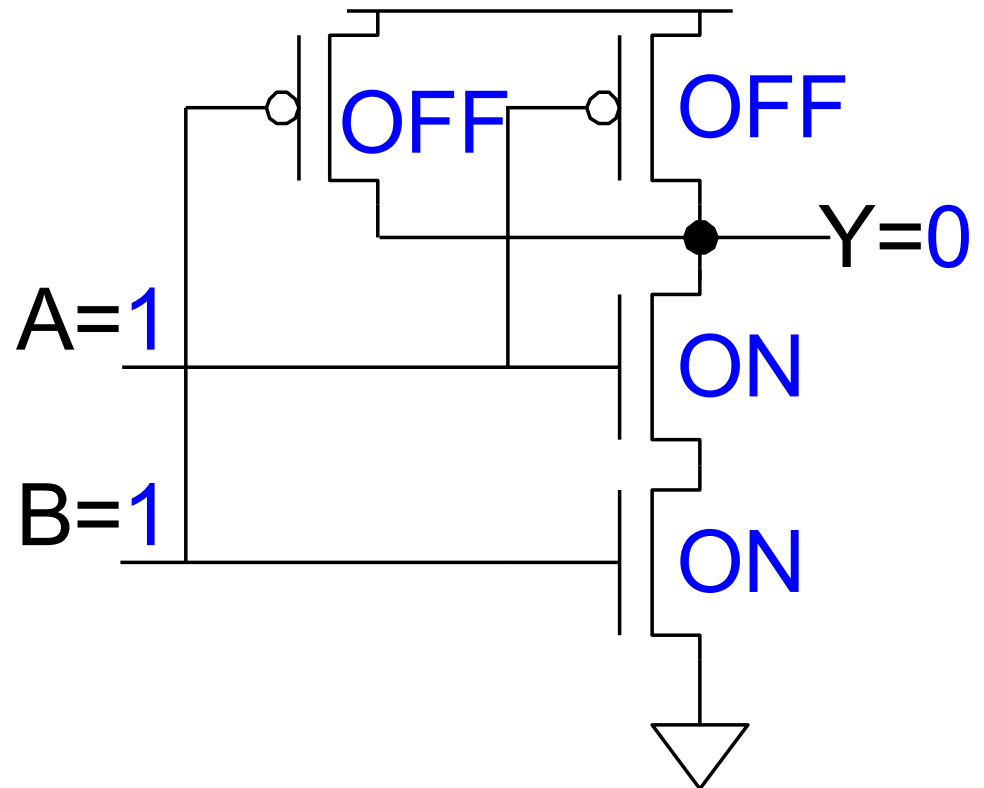 

# CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  

## 3-input NAND Gate

---

- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0





# CMOS Logic Gate Design

# Review CMOS Inverter



---

A	Y
0	1
1	0

  
  
# Complementary CMOS

- **Complementary** CMOS logic gates
  - nMOS *pull-down network*
  - pMOS *pull-up network*




	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)



 
## Construction of PDN

- NMOS devices in **series** implement a NAND function




 - NMOS devices in **parallel** implement a NOR function



 
# Series and Parallel (1)

- *Series*: both must be ON to be conductive
- *Parallel*: either can be ON to be conductive


 
## Series and Parallel (2)


- *Series*: both must be ON to be conductive
- *Parallel*: either can be ON to be conductive


 
# Conduction Complement

---

- Complementary CMOS gates always produce **0 or 1**
- Ex: NAND gate
  - Series nMOS:  **$Y=0$**  when both inputs are **1**
  - Thus  $Y=1$  when **either** input is 0
  - Requires **parallel** pMOS
- Rule of ***Conduction Complements***
  - Pull-up network is complement of pull-down
  - **Parallel -> series, series -> parallel**



## 4-input CMOS NOR gate


---

- Activity:
  - Sketch a 4-input CMOS NOR gate
 
# 4-input CMOS NOR gate


---

- Activity:
  - Sketch a 4-input CMOS NOR gate


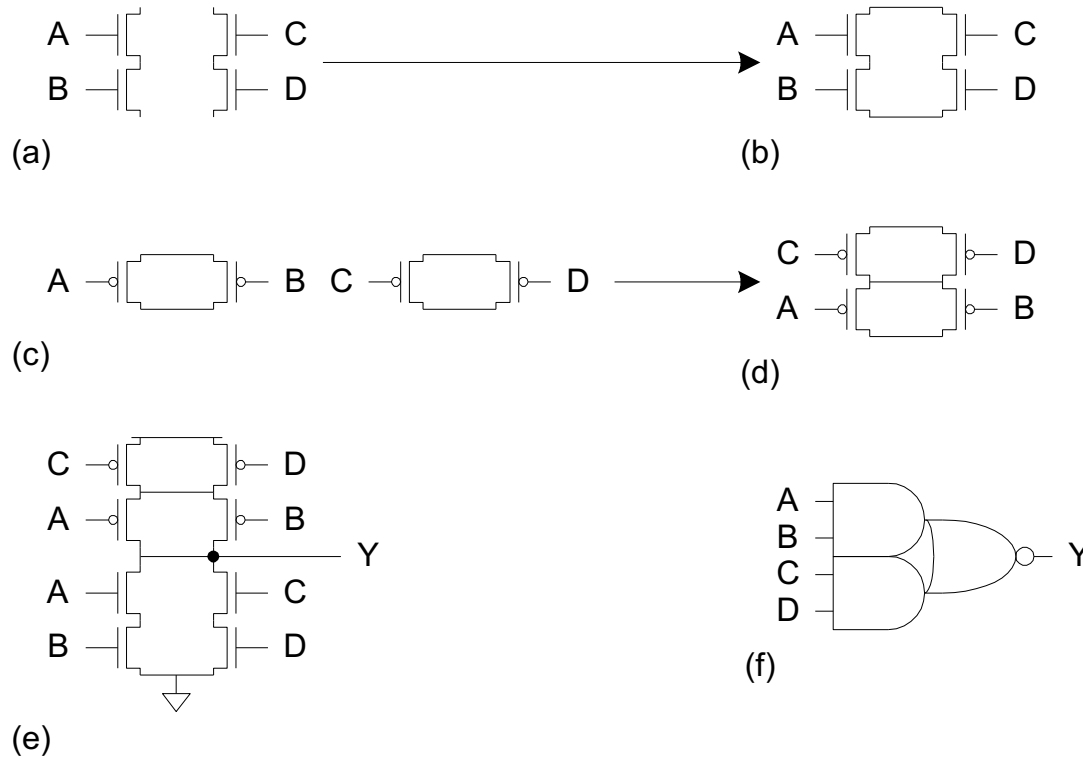
# Compound Gates

- *Compound gates* can do any inverting function
- Ex: AND-OR-INVERT, AOI22  $Y = \overline{A \cdot B + C \cdot D}$



## Example: O3AI


---

- $$Y = \overline{(A + B + C)} \cdot D$$




## Example: O3AI

- $$Y = \overline{(A + B + C)} \cdot D$$

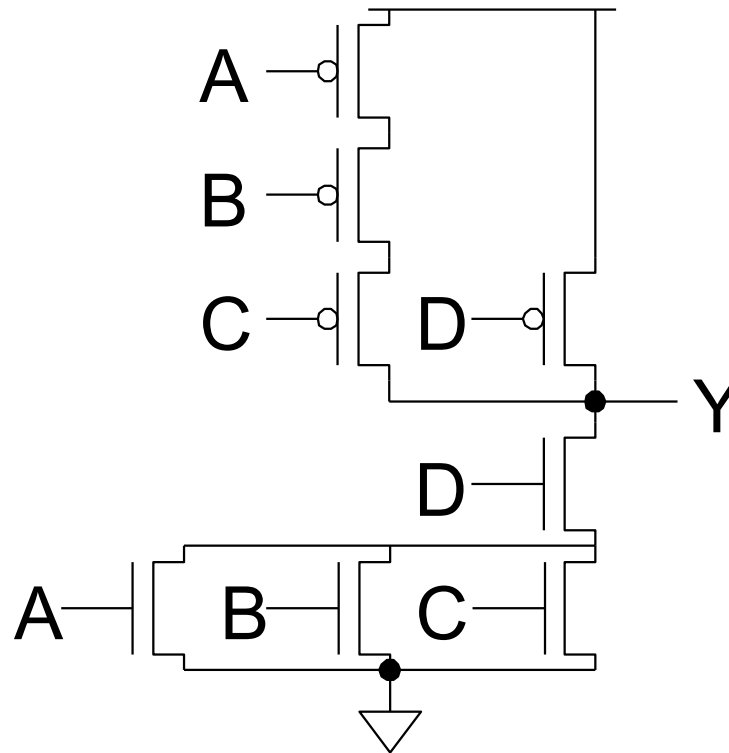

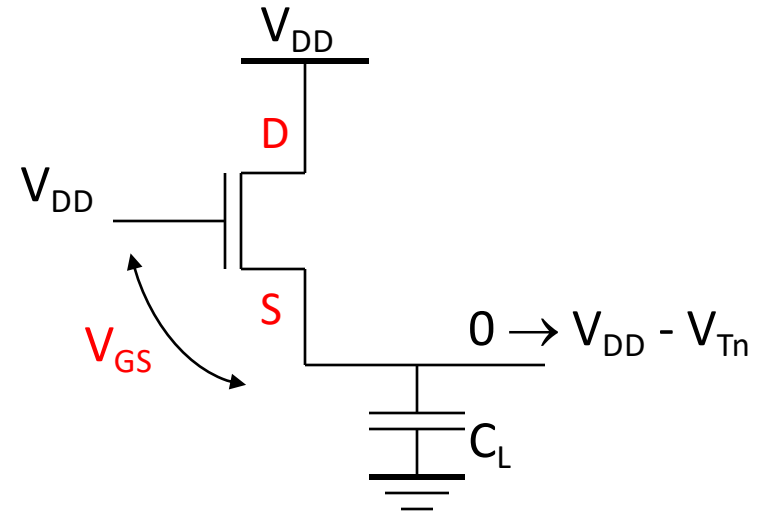
# Signal Strength

- **Strength of signal:** How close it approximates ideal voltage source
- $V_{DD}$  and GND rails are strongest 1 and 0
- nMOS pass **strong 0**
  - But degraded or weak 1
- pMOS pass **strong 1**
  - But degraded or weak 0
- Thus nMOS are best for pull-down network, pMOS are best for pull-up




**Weak "1"**

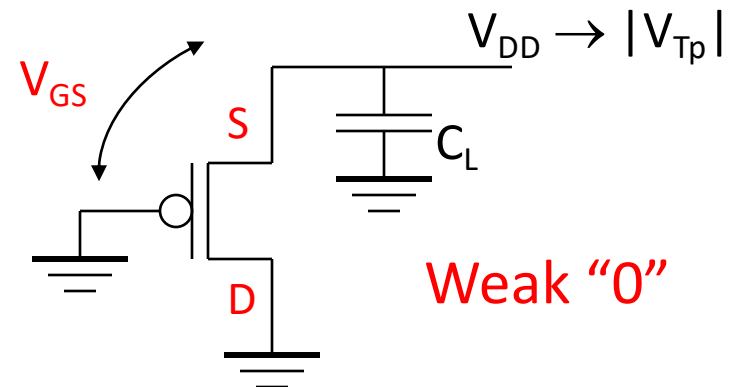


**Weak "0"**

# Review: Threshold Drops

PUN

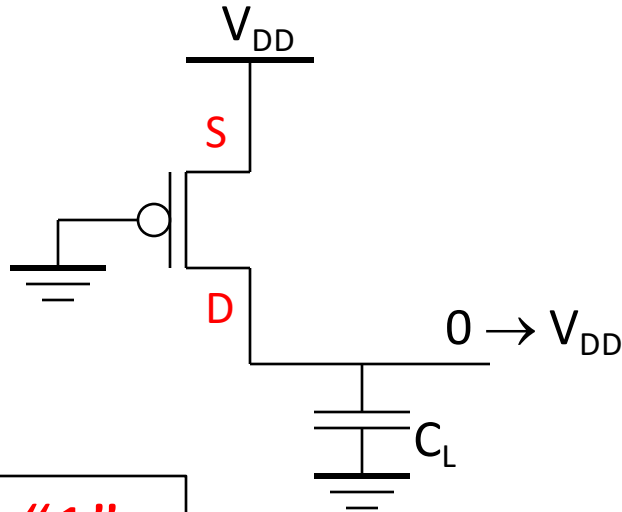


Strong "1"

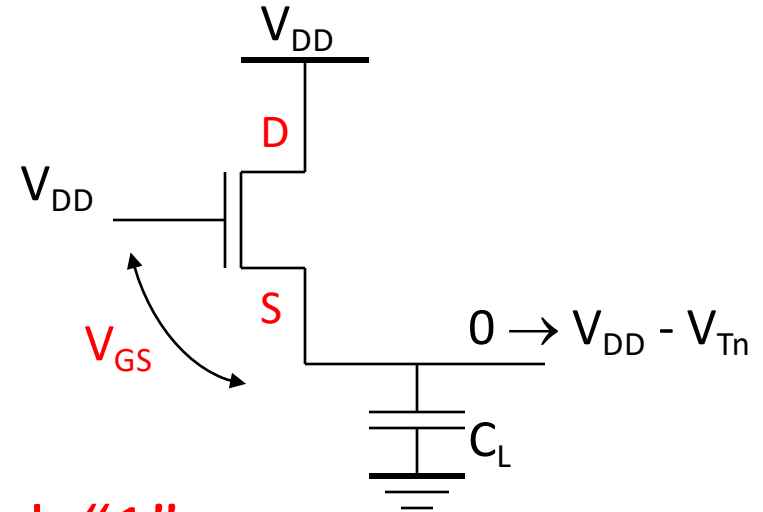


Weak "1"

PDN

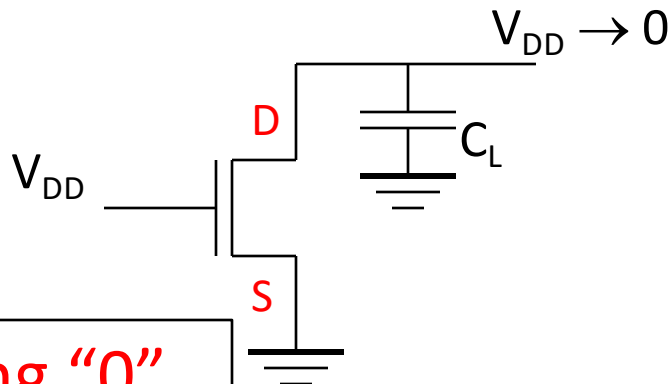










Strong "0"

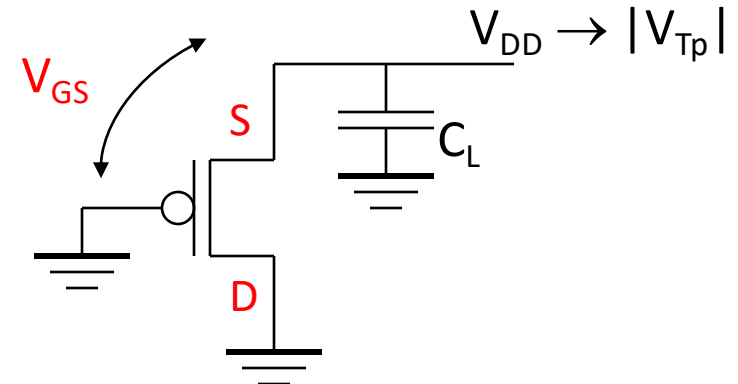

Weak "0"

         
# Pass Transistors

- Input is from the source
- Transistors can be used as switches


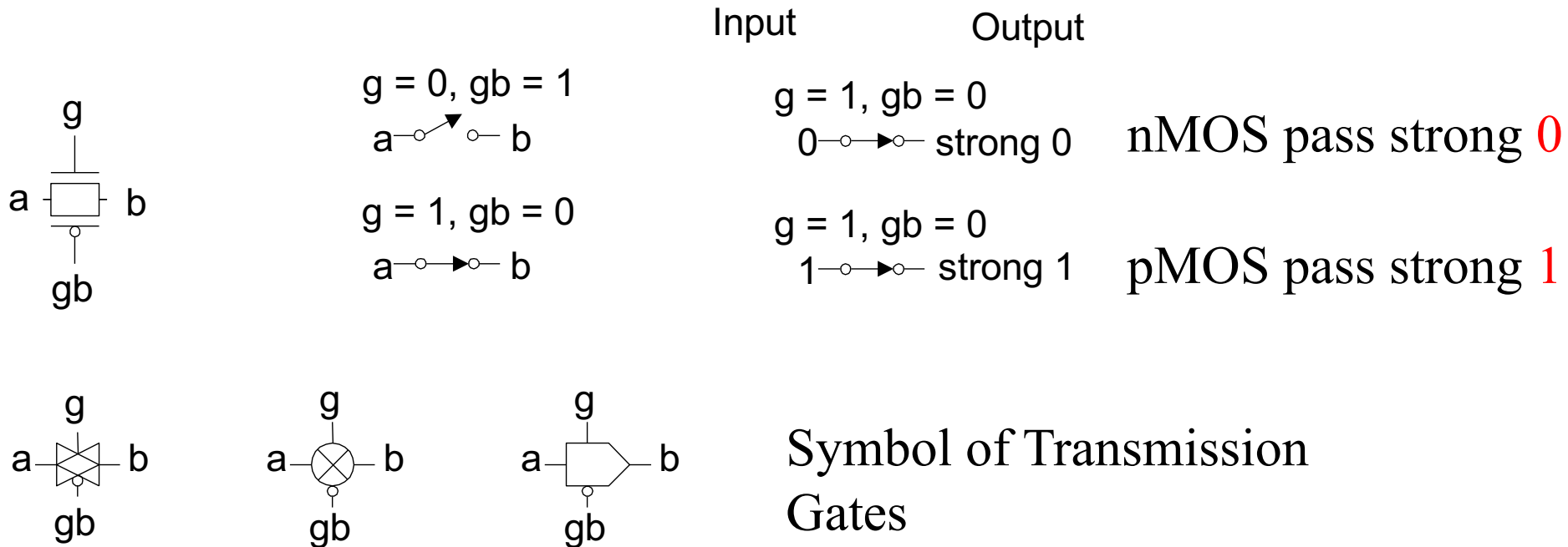
# Transmission Gates



- Pass transistors produce degraded outputs
- *Transmission gates* pass both strong 0 and 1



# Tristate buffer

- *Tristate buffer* produces Z when not enabled



EN	A	Y
0	0	
0	1	
1	0	
1	1	

  

# Tristate buffer


- *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  
 
# Nonrestoring Tristate

- Transmission gate acts as tristate buffer
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y




EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1


 
# Tristate Inverter


- Tristate inverter that produces **restored** output
  - Restored output: output is strongly driven and noise in the input is not passed to output
  - Violates **conduction complement** rule because we want a **Z** output



# Multiplexers

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

 


# Multiplexers

---

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 

## Gate-Level Mux Design

---



- How many transistors are needed?

$$Y = SD_1 + \bar{S}D_0$$

# Gate-Level Mux Design

- How many transistors are needed? 20

$$Y = SD_1 + \bar{S}D_0$$

  

# Transmission Gate Mux

---


- **Nonrestoring** mux uses two transmission gates

# Transmission Gate Mux

---


- **Nonrestoring** mux uses two transmission gates

Only 4 transistors

 
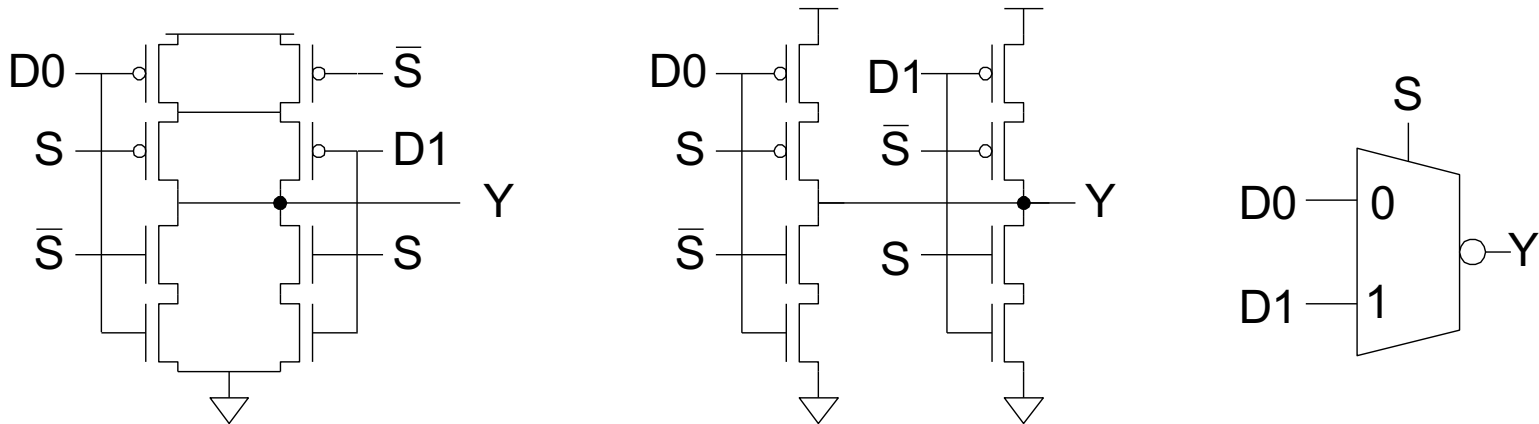
# Inverting Mux



- **Inverting** multiplexer
  - Use compound AOI22
  - Or pair of **tristate** inverters
  - Essentially the same thing
- **Noninverting** multiplexer adds an **inverter**






# 4:1 Multiplexer

  - 4:1 mux chooses one of 4 inputs using two selects
  - Two levels of 2:1 muxes
  - Or four tristates




 
# D Latch

- When CLK = **1**, latch is *transparent*
  - D flows through to Q like a buffer
- When CLK = **0**, the latch is *opaque*
  - Q **holds its old value** independent of D
- a.k.a. *transparent latch* or *level-sensitive latch*






  
# D Latch Design

- **Multiplexer** chooses D or old Q
- See the D operation in the next slide




# D Latch Operation

    


 
# D Flip-flop

- When CLK **ris**es, D is copied to **Q**
- At all other times, Q **holds** its value
- a.k.a. *positive edge-triggered flip-flop*






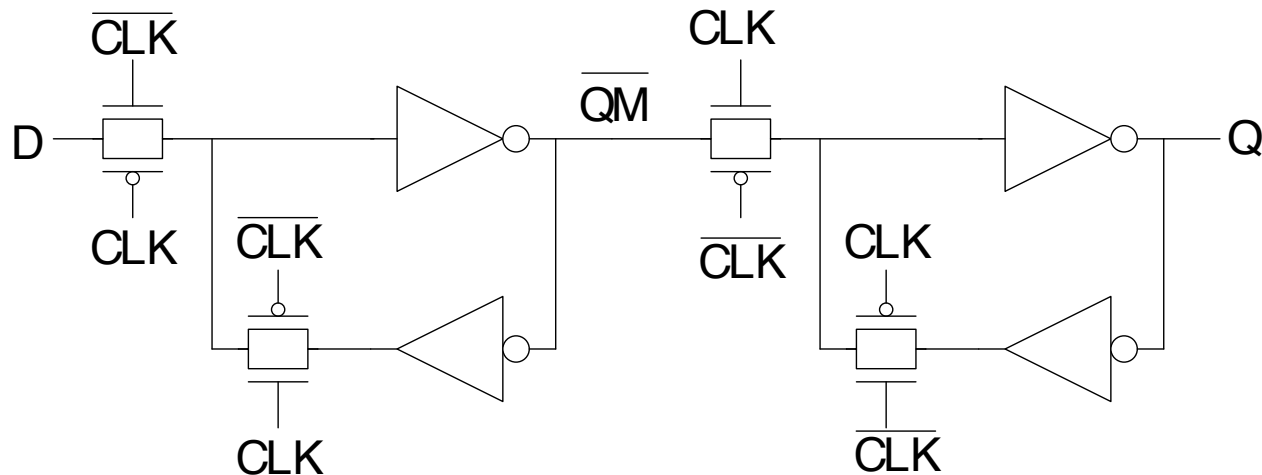 
# D Flip-flop Design

- Built from **master** and **slave** D latches



# D Flip-flop Operation

   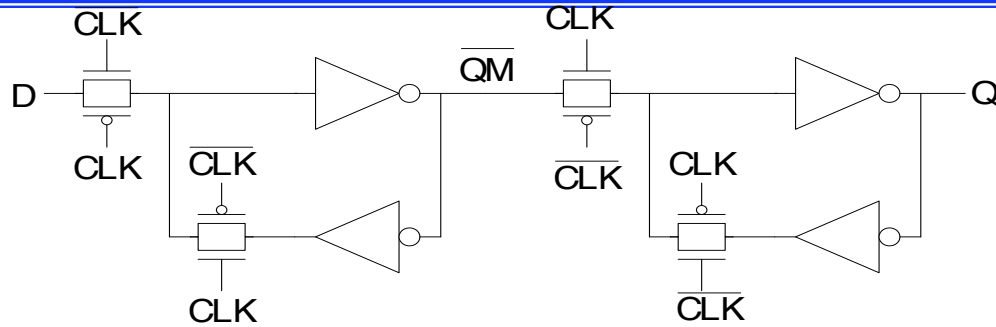

# Summary

---

- MOS Transistors are stack of **gate, oxide, silicon**
- Can be viewed as electrically controlled **switches**
- Build logic **gates** and flip-flops out of **switches**
- Now you know everything necessary to start designing schematics and layout for a simple chip!



## Backup slides